

Digital Integrated Circuits

YuZhuo Fu

contact:fuyuzhuo@ic.sjtu.edu.cn


Office location : 417 room

WeiDianZi building, No 800 DongChuan
road, MinHang Campus


Review content

- Format
 - Concept 40, Computing 60
 - 2++ hours
 - Mon. 8th 09:50-12:00
- Content
 - Introduction
 - Device
 - Inverter

Input&output resistance

 

Drive $\Rightarrow \infty$

 

Load $\Rightarrow 0$

Input&output resistance

- The voltage of the input signal comes, the gate could be regarded as load of front gate
- Set Empty load of current gate, calculate VI rate
- Input resistance

$$V_i = \frac{r_i}{R_s + r_i} V_s$$

Greater input resistance, signal transfer, less signal attenuation

- Output resistance


$$V_o = \frac{R_L}{r_o + R_L} V_o'$$

What is its meaning?

Less of the gate output resistance, smaller affect with load

Input(drive) re. is more greater than output(load)

The Ideal Gate

 

$$R_i = \infty$$


$$R_o = 0$$

$$Fanout = \infty$$

$$NM_H = NM_L = V_{DD}/2$$

Complementary CMOS

 nMOS pull-down network
pMOS pull-up network
a.k.a. static CMOS




- CMOS circuit layout/stick diagram
- Why NMOS/PDN PMOS/PUN

Device

- All state and principle
- Velocity saturation
- I-V formula (Hight-K Low-K material)
- Gate Capacitance

Current-Voltage Relations

The Deep-Submicron Era

 

Attention : velocity position

$$\mu_n = 3800 \text{ cm}^2/\text{V.s}, \mu_p = 1800 \text{ cm}^2/\text{V.s}$$

Charge per unit area: $Q_i(x) = -C_{ox}[V_{gs} - V(x) - V_T]$

$$I_D = -v_n(x)Q_i(x)W$$


$$v_n(x) = \mu_n E(x) = \mu_n \frac{dV}{dx}$$

$$I_D = \mu_n \frac{dV}{dx} C_{ox} [V_{gs} - V(x) - V_T] W$$

$$\int_0^L I_D dx = \int_0^{V_{DS}} \mu_n C_{ox} [V_{gs} - V(x) - V_T] W dV$$

$$I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_T) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right] \kappa(V_{DSAT})$$

A unified model for manual analysis

 

$$I_D = 0 \text{ for } V_{GT} \leq 0$$

$$I_D = k' \frac{W}{L} \left(V_{GT} V_{min} - \frac{V_{min}^2}{2} \right) (1 + \lambda V_{DS}) \text{ for } V_{GT} \geq 0$$

$$\text{with } V_{min} = \min(V_{GT}, V_{DS}, V_{DSAT}),$$


$$V_{GT} = V_{GS} - V_T,$$

$$\text{and } V_T = V_{T0} + \gamma (\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|-2\phi_F|})$$

Table 3.2 Parameters for manual model of generic 0.25 μm CMOS process (minimum length device).


| | V_{T0} (V) | γ ($\text{V}^{0.5}$) | V_{DSAT} (V) | k' (A/V^2) | λ (V^{-1}) |
|------|--------------|-------------------------------|----------------|-------------------------|-------------------------------|
| NMOS | 0.43 | 0.4 | 0.63 | 115×10^{-6} | 0.06 |
| PMOS | -0.4 | -0.4 | -1 | -30×10^{-6} | -0.1 |

Simple Model versus SPICE

 


Capacitance components

 - MOS structure capacitances
 - Overlap cap.
- Channel capacitances
 - Gate-body cap.
 - Gate-source cap.
 - Gate-drain cap.
- Junction/diffusion capacitances
 - Bottom-plate cap.
 - Side-well cap.



Gate channel Capacitance

 


| Operation Region | C_{gh} | C_{gs} | C_{gd} |
|------------------|------------------|-----------------------|--------------------|
| Cutoff | $C_{ox}WL_{eff}$ | 0 | 0 |
| Triode | 0 | $C_{ox}WL_{eff}/2$ | $C_{ox}WL_{eff}/2$ |
| Saturation | 0 | $(2/3)C_{ox}WL_{eff}$ | 0 |


on

Most important regions in digital design: saturation and cut-off

Gate Capacitance

 

 Capacitance as a function of V_{GS}
(with $V_{DS} = 0$)




Capacitance as a function of
the degree of saturation



CMOS static behavior

- *CMOS threshold voltage*
- *CMOS noise margin*
- *CMOS gain*
- *DC robust*
- *Inverter Chain*
- *Power*

CMOS Inverter Load Characteristics

 

CMOS Inverter VTC

  

Summary of CMOS inverter operation

| Region | Condition | P-device | N-device | output |
|--------|---------------------------------|-----------|-----------|-------------|
| A | $[0, V_{tn}]$ | linear | cutoff | V_{DD} |
| B | $[V_{tn}, V_{DD}/2]$ | linear | saturated | $V_{DD}/2$ |
| C | $=V_{DD}/2$ | saturated | saturated | X drop |
| D | $[V_{DD}/2, V_{DD} - V_{tp}]$ | saturated | linear | $<V_{DD}/2$ |
| E | $[V_{DD} - V_{tp} , V_{DD}]$ | cutoff | linear | 0 |

Switching Threshold as a function of Transistor Ratio

$$I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_T) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right] = V_{sat} C_{ox} W \left[V_{GS} - V_T - \frac{V_{DSAT}}{2} \right]$$

$$k_n V_{DSAT_n} (V_M - V_{Tn} - \frac{V_{DSAT_n}}{2}) + k_p V_{DSAT_p} (V_M - V_{DD} - V_{Tp} - \frac{V_{DSAT_p}}{2}) = 0$$

$$V_M = \frac{(V_{Tn} + \frac{V_{DSAT_n}}{2}) + r(V_{DD} + V_{Tp} + \frac{V_{DSAT_p}}{2})}{1 + r} \quad r = \frac{k_p V_{DSAT_p}}{k_n V_{DSAT_n}}$$

$$V_M \approx \frac{r V_{DD}}{1 + r}$$

$$\frac{(W/L)_p}{(W/L)_n} = \frac{k'_n V_{DSAT_n} (V_M - V_{Tn} - \frac{V_{DSAT_n}}{2})}{k'_p V_{DSAT_p} (V_{DD} - V_M + V_{Tp} + \frac{V_{DSAT_p}}{2})}$$

Switching threshold of CMOS inverter

Parameters for manual model of generic 0.25um CMOS process(minimum length device)

| | $V_{T0}(V)$ | $\gamma(V^{0.5})$ | $V_{DSAT}(V)$ | $k'(A/V^2)$ | $\lambda(V^{-1})$ |
|-------------|-------------|-------------------|---------------|----------------------|-------------------|
| <i>NMOS</i> | 0.43 | 0.4 | 0.63 | 115×10^{-6} | 0.06 |
| <i>PMOS</i> | -0.4 | -0.4 | -1 | -30×10^{-6} | -0.1 |

Assuming $W_p/W_n=8$, calculating $V_M=?$

$$r = \frac{k'_p \frac{W_p}{L_p} V_{DSAT_p}}{k'_n \frac{W_n}{L_n} V_{DSAT_n}} = \frac{-30 * (-1)}{115 * 0.63} * 8 = 3.3$$

$$V_M = \frac{(V_{Tn} + \frac{V_{DSAT_n}}{2}) + r(V_{DD} + V_{Tp} + \frac{V_{DSAT_p}}{2})}{1 + r}$$

$$= \frac{(0.43 + \frac{0.63}{2}) + 3.3(2.5 - 0.4 - \frac{0.4}{2})}{1 + 3.3} = \frac{0.75 + 3.3 * 1.9}{1 + 3.3} = 1.63V$$

Switching threshold of CMOS inverter

Parameters for manual model of generic 0.25um CMOS process(minimum length device)


| | $V_{T0}(V)$ | $\gamma(V^{0.5})$ | $V_{DSAT}(V)$ | $k'(A/V^2)$ | $\lambda(V^{-1})$ |
|-------------|-------------|-------------------|---------------|----------------------|-------------------|
| <i>NMOS</i> | 0.43 | 0.4 | 0.63 | 115×10^{-6} | 0.06 |
| <i>PMOS</i> | -0.4 | -0.4 | -1 | -30×10^{-6} | -0.1 |

$$\frac{(W/L)_p}{(W/L)_n} = \frac{k'_n V_{DSAT_n} (V_M - V_{Tn} - \frac{V_{DSAT_n}}{2})}{-k'_p V_{DSAT_p} (V_{DD} - V_M + V_{Tp} + \frac{V_{DSAT_p}}{2})} = \frac{115 \times 10^{-6} \times 0.63 \times (1.25 - 0.43 - \frac{0.63}{2})}{30 \times 10^{-6} \times 1 \times (1.25 - 0.4 - \frac{1}{2})} = 3.5$$

This rate let $V_M = V_{dd}/2$!

Determining V_{IH} and V_{IL}

A simplified approach!

 

$$V_{IH} - V_{IL} = -\frac{(V_{OH} - V_{OL})}{g} = \frac{-V_{DD}}{g}$$

$$V_{IH} = V_M - \frac{V_M}{g}, V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

$$NM_H = V_{DD} - V_{IH}, NM_L = V_{IL}$$

Example

$g=-30$, $V_{dd}=2.5V$, $V_M=1.0V$ Please estimate NM_H and NM_L

$$V_{IH} = V_M - V_M/G = 1.0 * (1 + 1/30) = 1.03V$$

$$V_{IL} = (V_{DD} - V_M)/G + V_M = -1.5/30 + 1.0 = 0.95V$$

$$NM_H = V_{OH} - V_{IH} = 2.5 - 1.03 = 1.47V$$


$$NM_L = V_{IL} - V_{OL} = 0.95V$$

Inverter Gain

$$\begin{aligned}
 g &= \left. \frac{dV_{out}}{dV_{in}} \right|_{V_{in}=V_M} \\
 &= - \left. \frac{k_n V_{DSATn} (1 + \lambda_n V_{out}) + k_p V_{DSATp} (1 + \lambda_p V_{out} - \lambda_p V_{DD})}{\lambda_n k_n V_{DSATn} (V_{in} - V_{Tn} - V_{DSATn}/2) + \lambda_p k_p V_{DSATp} (V_{in} - V_{DD} - V_{Tp} - V_{DSATp}/2)} \right|_{V_{in}=V_M} \\
 &\approx - \frac{k_n V_{DSATn} (1 + \lambda_n V_{out}) + k_p V_{DSATp} (1 + \lambda_p V_{out} - \lambda_p V_{DD})}{k_n V_{DSATn} (V_{in} - V_{Tn} - V_{DSATn}/2) (\lambda_n - \lambda_p)} \\
 &= - \frac{1 + \gamma}{(V_M - V_{Tn} - V_{DSATn}/2) (\lambda_n - \lambda_p)}
 \end{aligned}$$

Ratio increase, Gain increase
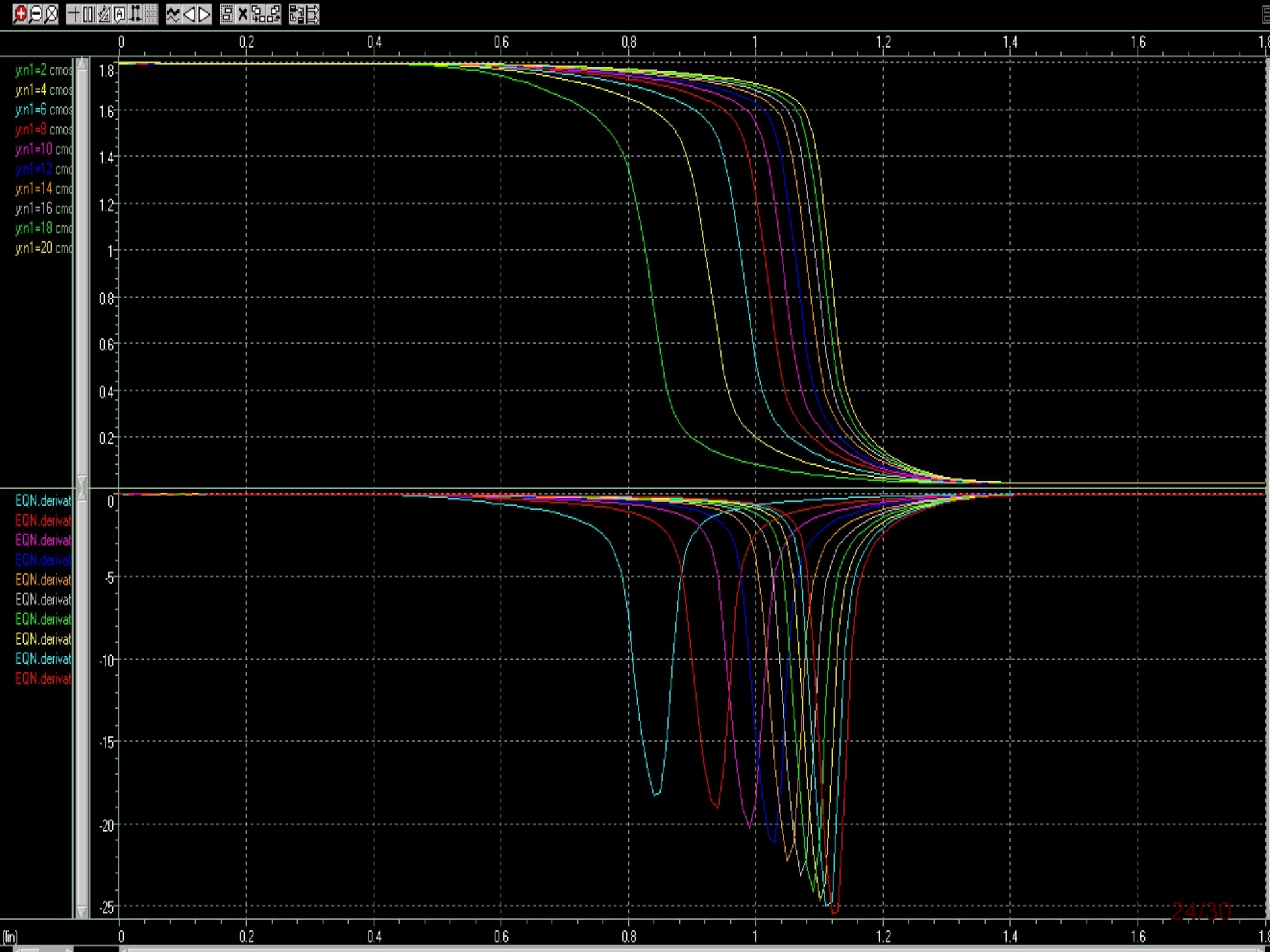
$$\gamma = \frac{k'_p \frac{W_p}{L_p} V_{DSATp}}{k'_n \frac{W_n}{L_n} V_{DSATn}}$$



An example

An inverter in the generic 0.25um CMOS technology designed with a PMOS-to-NMOS ratio of 3.4 and with the NMOS transistor minimum size ($W=0.375\mu\text{m}$, $L=0.25\mu\text{m}$, $W/L=1.5$), $V_{dd}=2.5\text{V}$, Please give the gain of V_M , and V_{IL} , V_{IH} , NM_L , NM_H , VTC curve

Parameters for manual model of generic 0.25um CMOS process(minimum length device)

| | $V_{TD}(V)$ | $\gamma(V^{0.5})$ | $V_{DSAT}(V)$ | $K'(A/V^2)$ | $\lambda(V^{-1})$ |
|------|-------------|-------------------|---------------|----------------------|-------------------|
| NMOS | 0.43 | 0.4 | 0.63 | 115×10^{-6} | 0.06 |
| PMOS | -0.4 | -0.4 | -1 | -30×10^{-6} | -0.1 |

$$\gamma = \frac{k'_p W_p / L_p V_{DSATp}}{k'_n W_n / L_n V_{DSATn}} = \frac{-30 * (-1)}{115 * 0.63} * 3.4 = 1.4$$

$$g \approx - \frac{1 + \gamma}{\left(V_M - V_{Tn} - \frac{V_{DSATn}}{2} \right) (\lambda_n - \lambda_p)} = - \frac{1 + 1.4}{\left(1.25 - 0.43 - \frac{0.63}{2} \right) (0.06 + 0.1)}$$

$$= - \frac{2.4}{0.505 * 0.16} = -30$$

tpHL/tpLH

Computing the Capacitances


 


Figure 1

| capacitor | expression | Value(fF) (H->L) | Value(fF) (L->H) |
|-----------|--|---------------------|---------------------|
| C_{gd1} | $2C_{GD0n} \cdot W_n$ | 0.23 | 0.23 |
| C_{gd2} | $2C_{GD0p} \cdot W_p$ | 0.61 | 0.61 |
| C_{db1} | $K_{eqn}AD_nC_J + K_{eqwn}PD_nC_{JSW}$ | 0.66 | 0.90 |
| C_{db2} | $K_{eqn}AD_nC_J + K_{eqwn}PD_nC_{JSW}$ | 1.5 | 1.15 |
| C_{g3} | $(C_{GD0n} + C_{GSO_n})W_n + C_{ox}W_nL_n$ | 0.76 | 0.76 |
| C_{g4} | $(C_{GD0p} + C_{GSO_p})W_p + C_{ox}W_pL_p$ | 2.28 | 2.28 |
| C_w | | 0.12 | 0.12 |
| C_L | | 6.1 | 6.0 |

Table 1

Inverter Chain

 

If C_L is given:

- How many stages are needed to minimize the delay?***
- How to size the inverters?***

CMOS Energy & Power Equations

$$E = C_L V_{DD}^2 P_{0 \rightarrow 1} + t_{sc} V_{DD} I_{peak} + V_{DD} I_{leakage} 1/f_{clock}$$

$$f_{0 \rightarrow 1} = P_{0 \rightarrow 1} * f_{clock}$$

$$P = C_L V_{DD}^2 f_{0 \rightarrow 1} + t_{sc} V_{DD} I_{peak} + V_{DD} I_{leakage}$$

Dynamic power

*Short-circuit
power*

Leakage power

Lowering Dynamic Power

Capacitance:
Function of fan-out, wire length, transistor sizes

Supply Voltage:
Has been dropping with successive generations

$$P_{\text{dyn}} = C_L V_{\text{DD}}^2 P_{0 \rightarrow 1} f$$

Activity factor:
How often, on average, do wires switch?

Clock frequency:
Increasing...

| Parameter | Relation | Full Scaling | General Scaling | Fixed Voltage Scaling |
|-------------------|------------------|--------------|-----------------|-----------------------|
| W, L, t_{ox} | | 1/S | 1/S | 1/S |
| V_{DD} , V_T | | 1/S | 1/U | 1 |
| N_{SUB} | V/W_{depl}^2 | S | S^2/U | S^2 |
| Area/Device | WL | $1/S^2$ | $1/S^2$ | $1/S^2$ |
| C_{ox} | $1/t_{ox}$ | S | S | S |
| C_L | $C_{ox}WL$ | 1/S | 1/S | 1/S |
| k_n , k_p | $C_{ox}W/L$ | S | S | S |
| I_{av} | $k_{n,p} V^2$ | 1/S | S/U^2 | S |
| t_p (intrinsic) | $C_L V / I_{av}$ | 1/S | U/S^2 | $1/S^2$ |
| P_{av} | $C_L V^2 / t_p$ | $1/S^2$ | S/U^3 | S |
| PDP | $C_L V^2$ | $1/S^3$ | $1/SU^2$ | 1/S |