

*Digital Integrated Circuits*  
***Designing***  
***Sequential Circuits***

***Fuyuzhuo***

# Sequential Logic Circuits

- **Introduction**
- **Timing**
- **Static Latches and Registers**
- **Dynamic Latches and Registers**

# Sequential Logic Circuits


- *Introduction*
- Timing
- Static Latches and Registers
- Dynamic Latches and Registers

**Comb.** or **Seq.**


 
# Sequencing

- *Combinational logic*
  - output depends on current inputs
- *Sequential logic*
  - output depends on current and previous inputs
  - Requires separating previous, current, future
  - Called *state* or *tokens*
  - Ex: FSM, pipeline



Finite State Machine

Digital IC


Pipeline

# Sequencing Elements


- **Latch:** Level sensitive
  - a.k.a. transparent latch, D latch
- **Flip-flop:** edge triggered
  - A.k.a. master-slave flip-flop, D flip-flop, D register

- **Timing Diagrams**

- Transparent
- Opaque
- Edge-trigger

 

# Sequential Logic

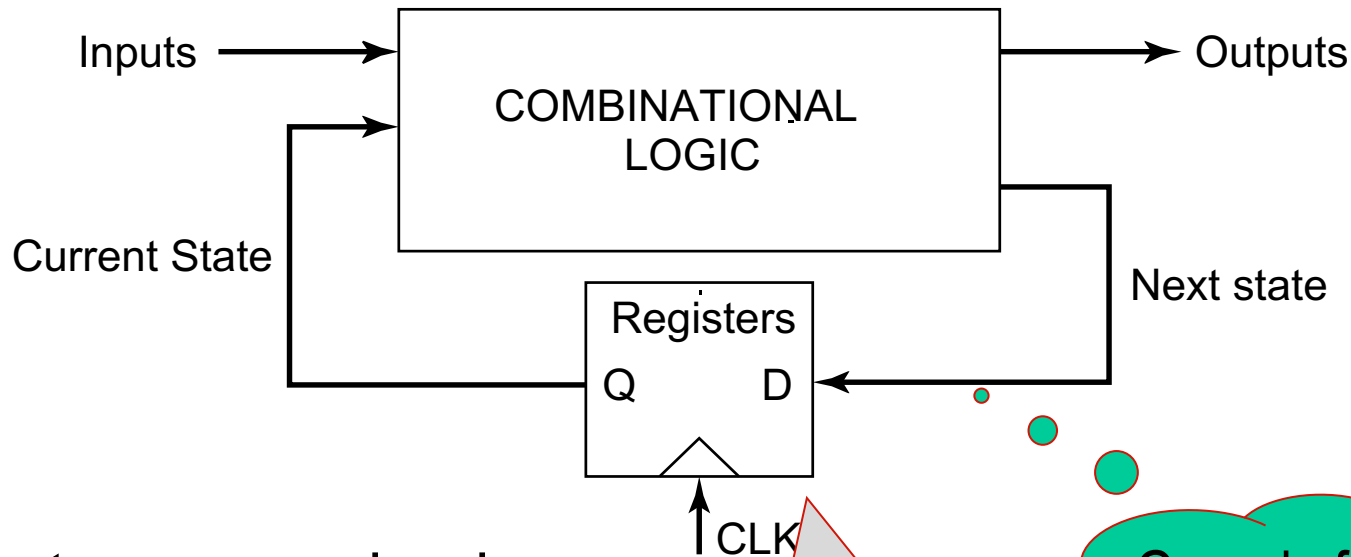


- 2 storage mechanisms
- positive feedback
  - charge-based

Generic finite-state machine

*Synchronous, rising/positive edge triggered, falling edge/negative edge triggered*

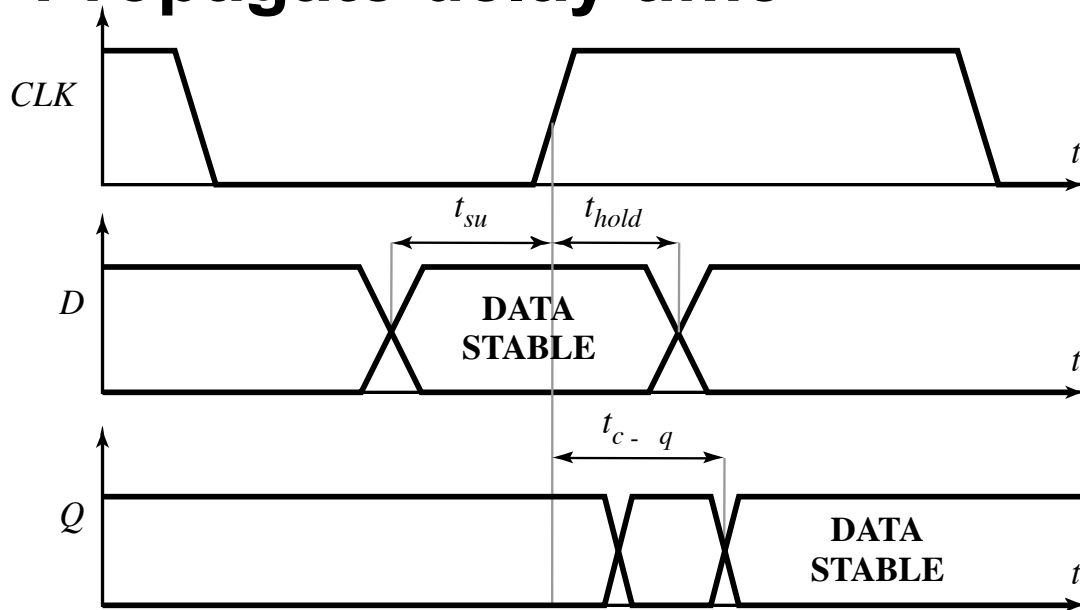
# Timing Definitions

- ❶ **Setup time:** the time that the data inputs must be valid before clock transition
- ❷ **hold time:** the time that the data must remain valid after the clock transition
- ❸ **Propagate delay time**




sequential logic


Digital IC

 

# Characterizing Timing

 

Register

 


Latch


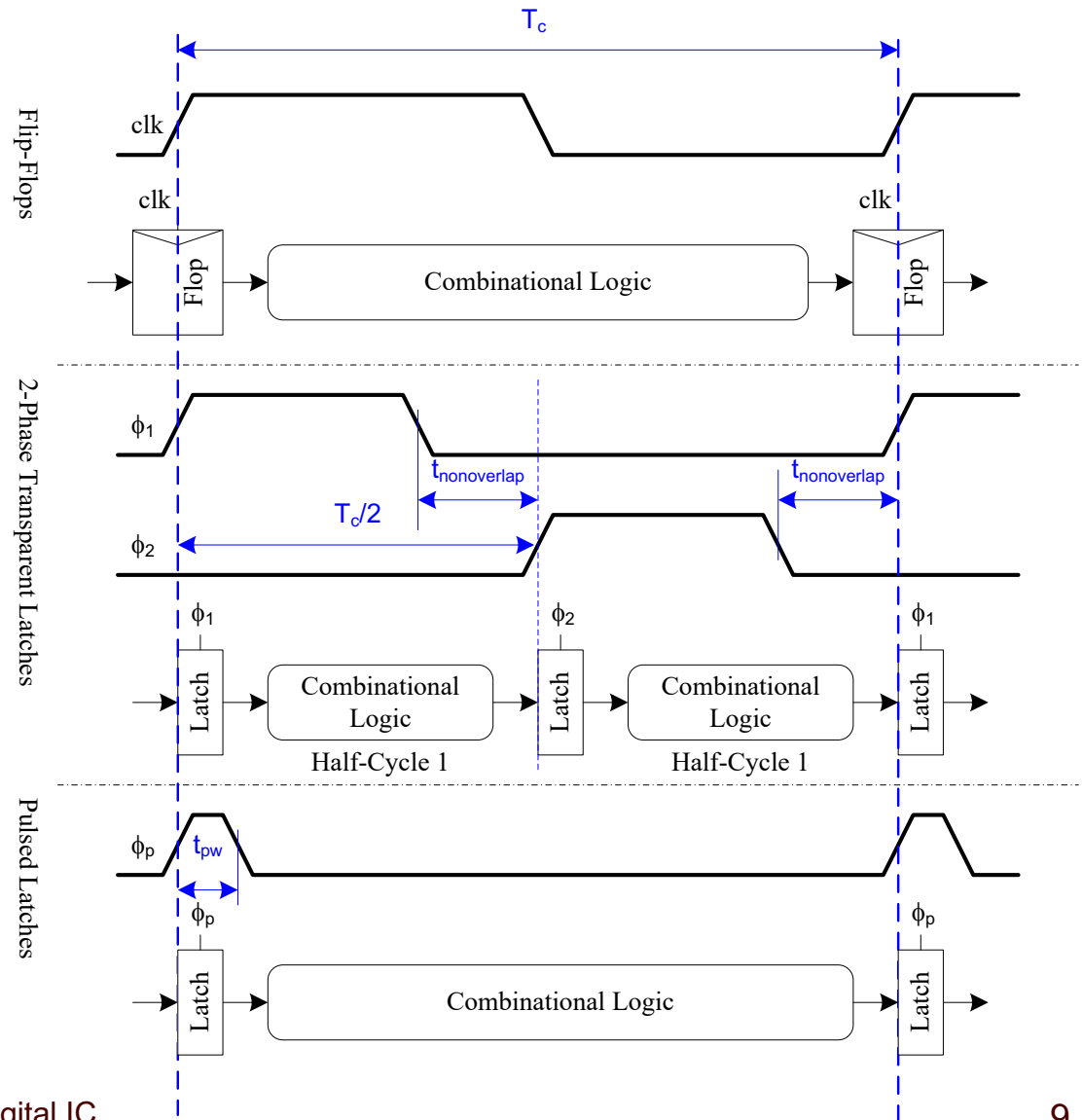
# Sequencing Methods

- Flip-flops
- 2-Phase Latches
- Pulsed Latches





# Design Sequential Logic Circuits

- Introduction
- ***Timing***
- Static Latches and Registers
- Dynamic Latches and Registers







# Timing Diagrams

## Contamination and Propagation Delays

  


$t_{pd}$	Logic Prop. Delay
$t_{cd}$	Logic Cont. Delay
$t_{pcq}$	Latch/Flop Clk-Q Prop Delay
$t_{ccq}$	Latch/Flop Clk-Q Cont. Delay
$t_{pdq}$	Latch D-Q Prop Delay
$t_{pcq}$	Latch D-Q Cont. Delay
$t_{setup}$	Latch/Flop Setup Time
$t_{hold}$	Latch/Flop Hold Time

    

 
# Max-Delay: Flip-Flops


$$t_{pd}^{\uparrow} < T_c^{\uparrow} - \underbrace{(t_{\text{setup}} + t_{pcq})}_{\text{sequencing overhead}}$$



# Max Delay: 2-Phase Latches

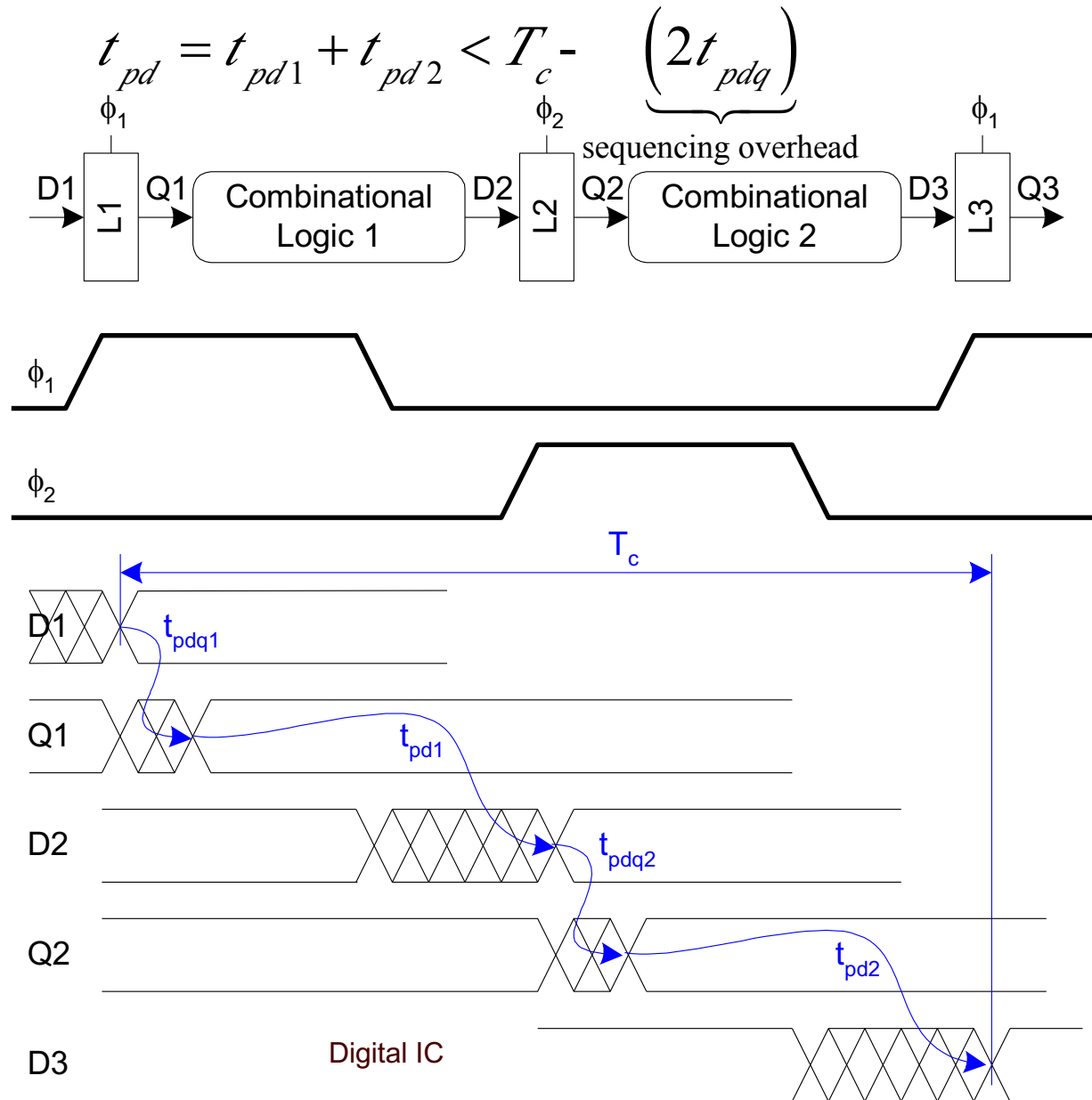

# Max Delay: Pulsed Latches

 

$$T_c \geq \max(t_{pdq} + t_{pd}, t_{pcq} + t_{pd} + t_{setup} - t_{pw})$$


$$t_{pd} = T_c - \max(t_{pdq}, t_{pcq} + t_{setup} - t_{pw})$$

sequential logic


Digital IC

Sequencing overhead


# Min-Delay: Flip-Flops

 

 *Race condition*  
*Hold time failure*  
*min-delay failure*


 
$$t_{cd} \geq t_{\text{hold}} - t_{ccq}$$




# Min-Delay: 2-Phase Latches

Hold time reduced by nonoverlap


Paradox: hold applies twice each cycle, vs. only once for flops.

But a flop is made of two latches!

 




# Min-Delay: Pulsed Latches

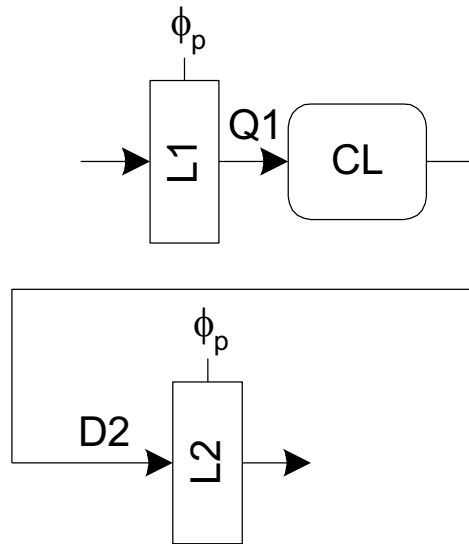

Hold time increased by pulse width

 
$$t_{cd} \geq t_{\text{hold}} - t_{ccq} + t_{pw}$$



# Clock skew

- Definition
  - The spatial variation in arrival time of a clock transition on an integrated circuit
- Sources
  - Static mismatches in the clock paths and differences in the clock load

# Positive/negative skew

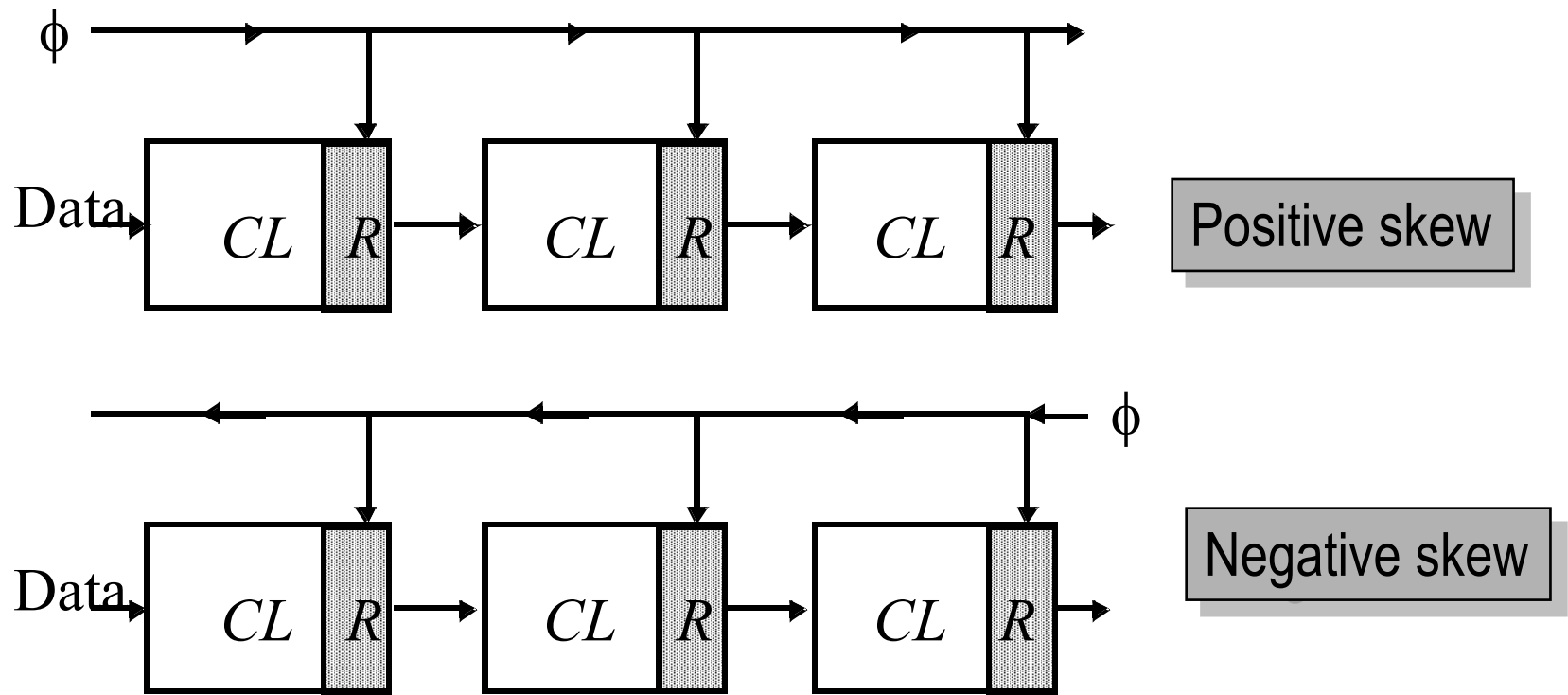

# Clock skew about FF

$$t_{pdq} \leq T_c - (t_{pcq} + t_{setup} + t_{skew})$$

*negative skew*


**Positive skew for better condition**

*Large is better !*

Ex.  $t_{pcq}=20ps, t_{setup}=30ps, T_c=300ps, t_{skew}=50ps$

$t_{pdq} \leq 300-20-30=250$ ,  $t_{pdq}=240$  is OK

 Including skew delay,  $t_{pdq} \leq 300-20-30-50=200ps$ ,  $t_{pdq}=240$  is not OK!



# Clock skew about FF

*Small is better !*


$$t_{cd} \geq t_{hold} - t_{ccq} + t_{skew}$$

**Positive skew for worse condition**



Ex.  $t_{cd}=20ps, t_{hold}=20ps, t_{ccq}=2ps, t_{skew}=5ps$

$t_{cd} \geq 20-2=18, t_{cd}=20$  is OK!

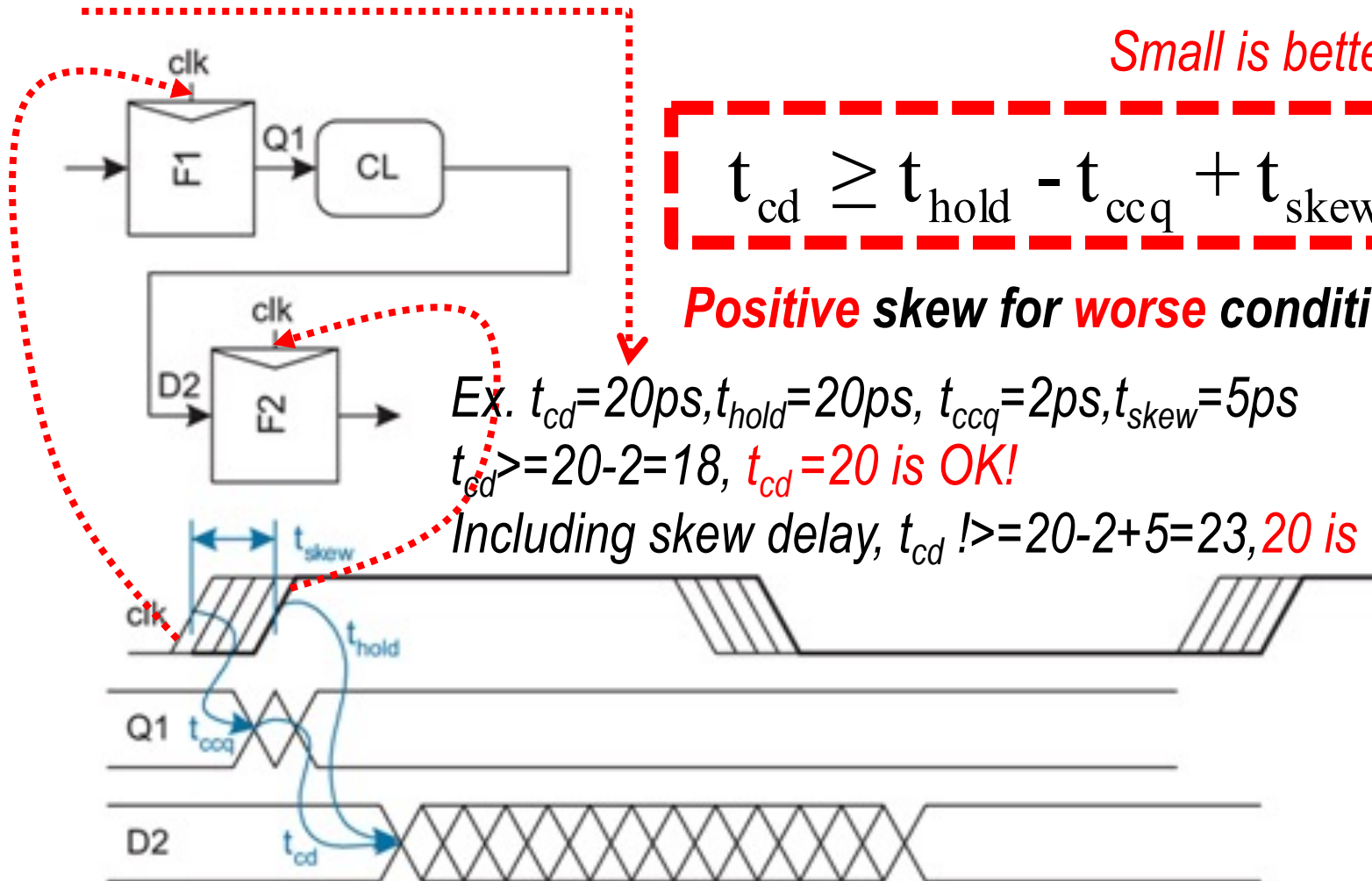Including skew delay,  $t_{cd} \geq 20-2+5=23, 20$  is Not OK




# Clock tree

  
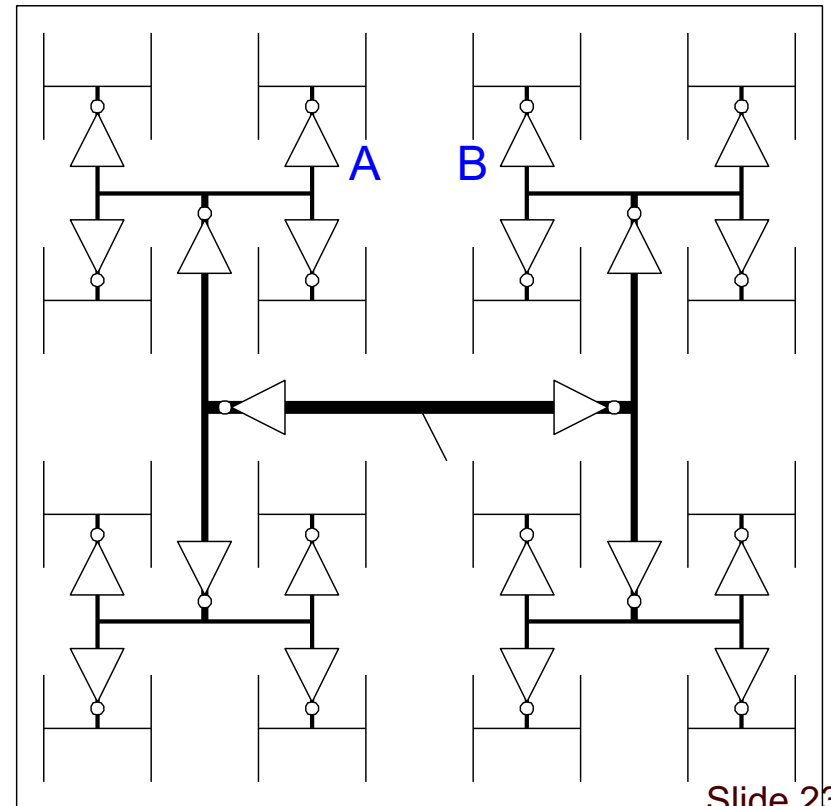
# H-Trees

- Fractal structure
  - Gets clock arbitrarily close to any point
  - Matched delay along all paths
- Delay variations cause skew
- A and B might see big skew



# Design Sequential Logic Circuits

- Introduction
- Timing
- ***Static Latches and Registers***
- Dynamic Latches and Registers





# Static vs Dynamic Storage

- Static storage
  - preserve state as long as the power is on
  - have positive feedback (**regeneration**)
  - useful when updates infrequent (clock gating)
- Dynamic storage
  - store state on parasitic capacitors
  - only hold state for short periods of time (ms)
  - require periodic refresh
  - usually simpler, higher speed , lower power


# Static Latches and Registers

- The bistability principle
- Multiplexer-based latches
- Master-slave edge-triggered register
- Low-voltage static latches
- Static SR Flip-flops-writing data by pure force


# Static Latches and Registers

- ***The bistability principle***
- Multiplexer-based latches
- Master-slave edge-triggered register
- Low-voltage static latches
- Static SR Flip-flops-writing data by pure force

# Review: The Regenerative Property

 


cascaded inverters

 


*If the gain in the transient region is larger than 1, only A and B are stable operation points. C is a metastable operation point.*
 
# Bistable Circuits

- The cross-coupling of two inverters results in a bistable circuit (a circuit with two stable states)
- Have to be able to change the stored value by making A (or B) temporarily unstable by increasing the loop gain to a value larger than 1
  - done by applying a trigger pulse at  $V_{i1}$  or  $V_{i2}$
  - the width of the trigger pulse need be only a little larger than the total propagation delay around the loop circuit (twice the delay of an inverter)






# SR Latch

 

S	R	Q	!Q	
0	0	Q	!Q	memory
1	0	1	0	set
0	1	0	1	reset
1	1	0	0	disallowed

Break the  
feedback

# Clocked D Latch

   


# Static Latches and Registers

- The bistability principle
- ***Multiplexer-based latches***
- Master-slave edge-triggered register
- Low-voltage static latches
- Static SR Flip-flops-writing data by pure force



 
# Mux-Based Latches

*Negative latch*  
(transparent when  $CLK = 0$ )



$$Q = Clk \cdot Q + \overline{Clk} \cdot In$$


 
*Positive latch*  
(transparent when  $CLK = 1$ )



$$Q = \overline{Clk} \cdot Q + Clk \cdot In$$
  
# Writing into a Static Latch


*Use the clock as a decoupling signal, that distinguishes between the **transparent** and **opaque** states*




*Converting into a MUX*

*Forcing the state (can implement as NMOS-only)*

# Mux-Based Latch

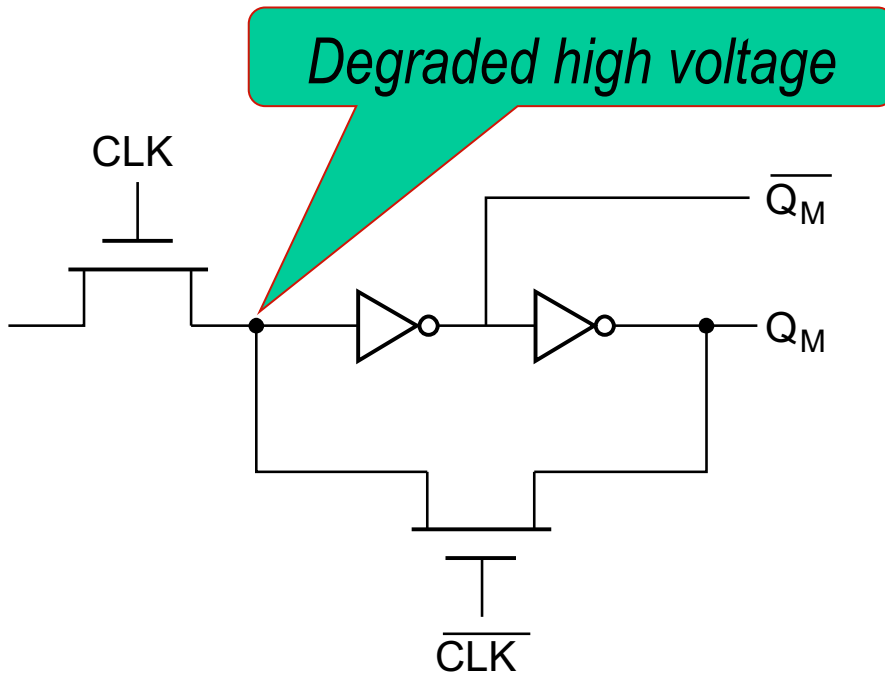


NMOS only

 

Non-overlapping clocks
 
# Latch Design


- Pass Transistor Latch
- Pros
  - + Tiny
  - + Low clock load
- Cons
  - $V_t$  drop
  - nonrestoring
  - backdriving
  - output noise sensitivity
  - dynamic
  - diffusion input



Used in 1970's

 
# Latch Design

- Transmission gate
  - + No  $V_t$  drop
  - Requires inverted clock



 
# Latch Design

- Inverting buffer
  - + Restoring
  - + No backdriving
  - + Fixes either
    - Output noise sensitivity
    - Or diffusion input
- Inverted output



 
# Latch Design

- Tristate feedback
  - + Static
    - Backdriving risk
- Static latches are now essential


 
# Latch Design


- Buffered input
  - + Fixes diffusion input
  - + Noninverting




 
# Latch Design


- Buffered output
  - + No backdriving
- Widely used in standard cells
  - + Very robust (most important)
  - Rather large
  - Rather slow (1.5 – 2 FO4 delays)
  - High clock loading



# Static Latches and Registers

- The bistability principle
- Multiplexer-based latches
- ***Master-slave edge-triggered register***
- Low-voltage static latches
- Static SR Flip-flops-writing data by pure force


# Master-Slave (Edge-Triggered) Register

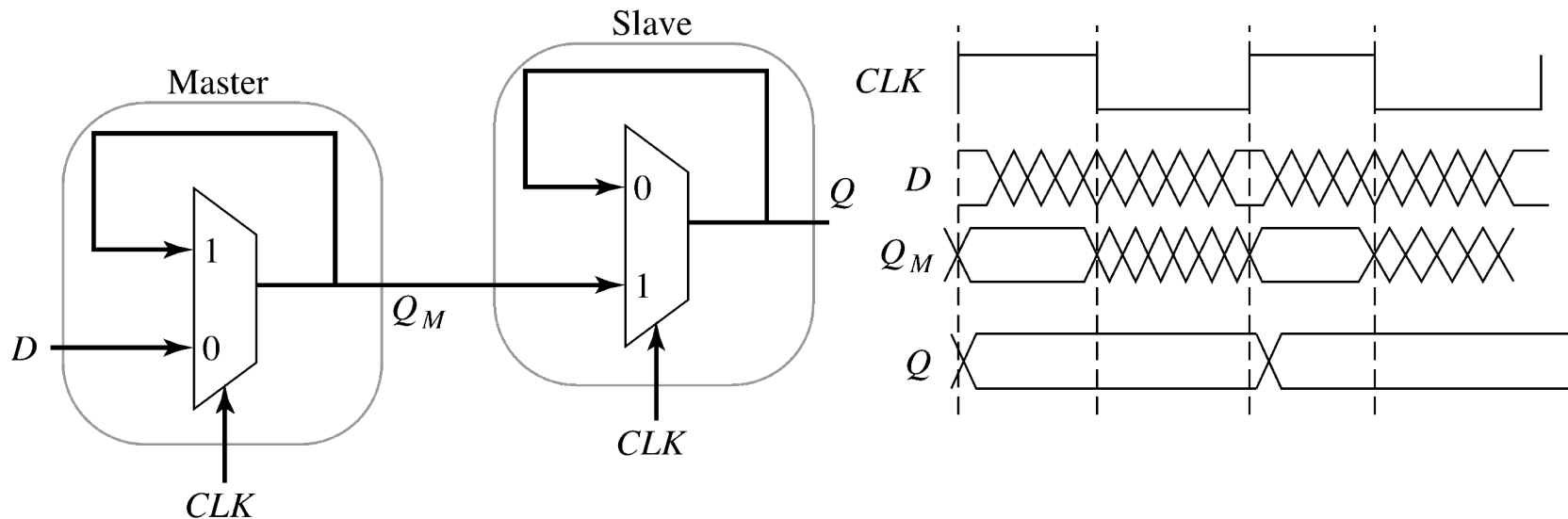


*Two opposite latches trigger on edge Also called master-slave latch pair*

# Master-Slave Register


*Multiplexer-based latch pair*

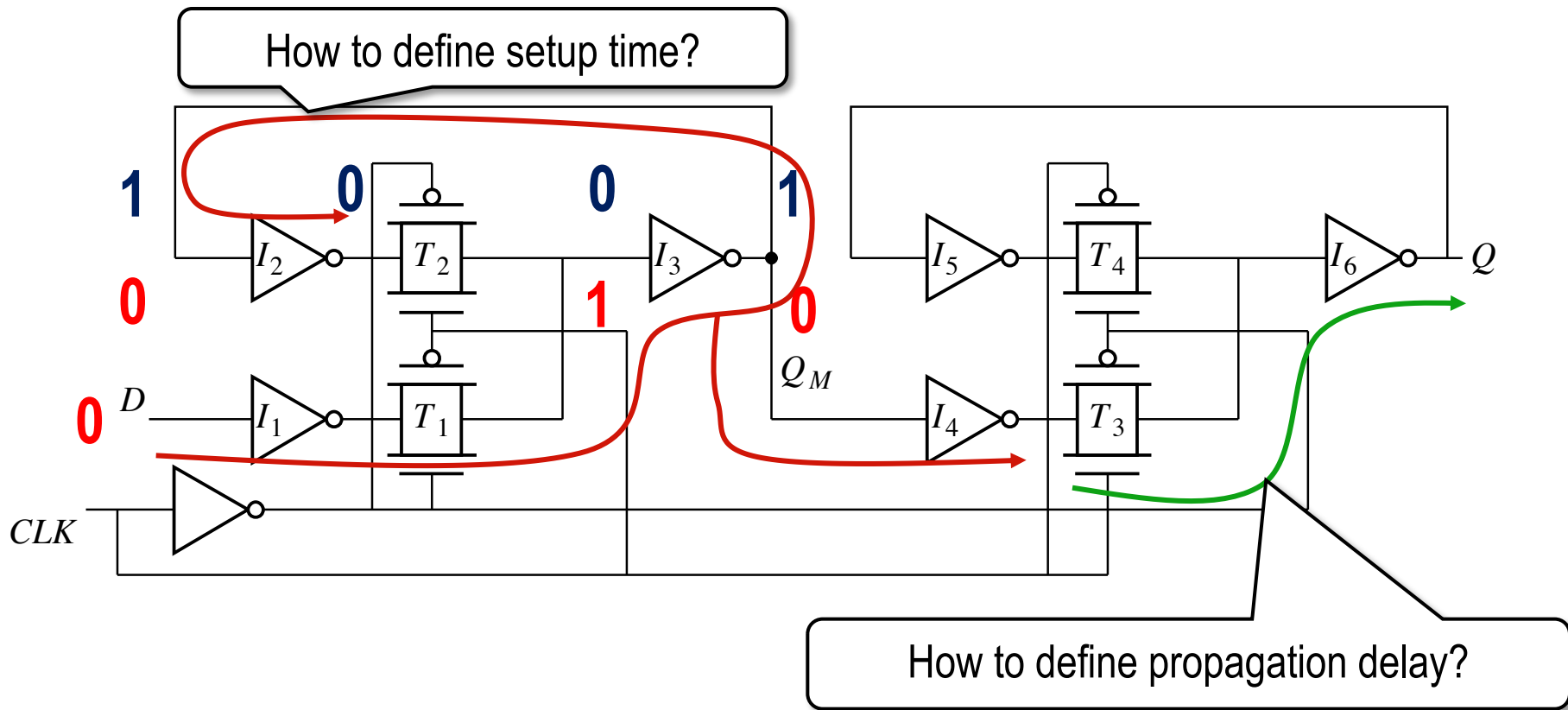


# Clk-Q Delay

 

# Setup Time

 


 (a)  $T_{\text{setup}} = 0.21 \text{ nsec}$





(b)  $T_{\text{setup}} = 0.20 \text{ nsec}$
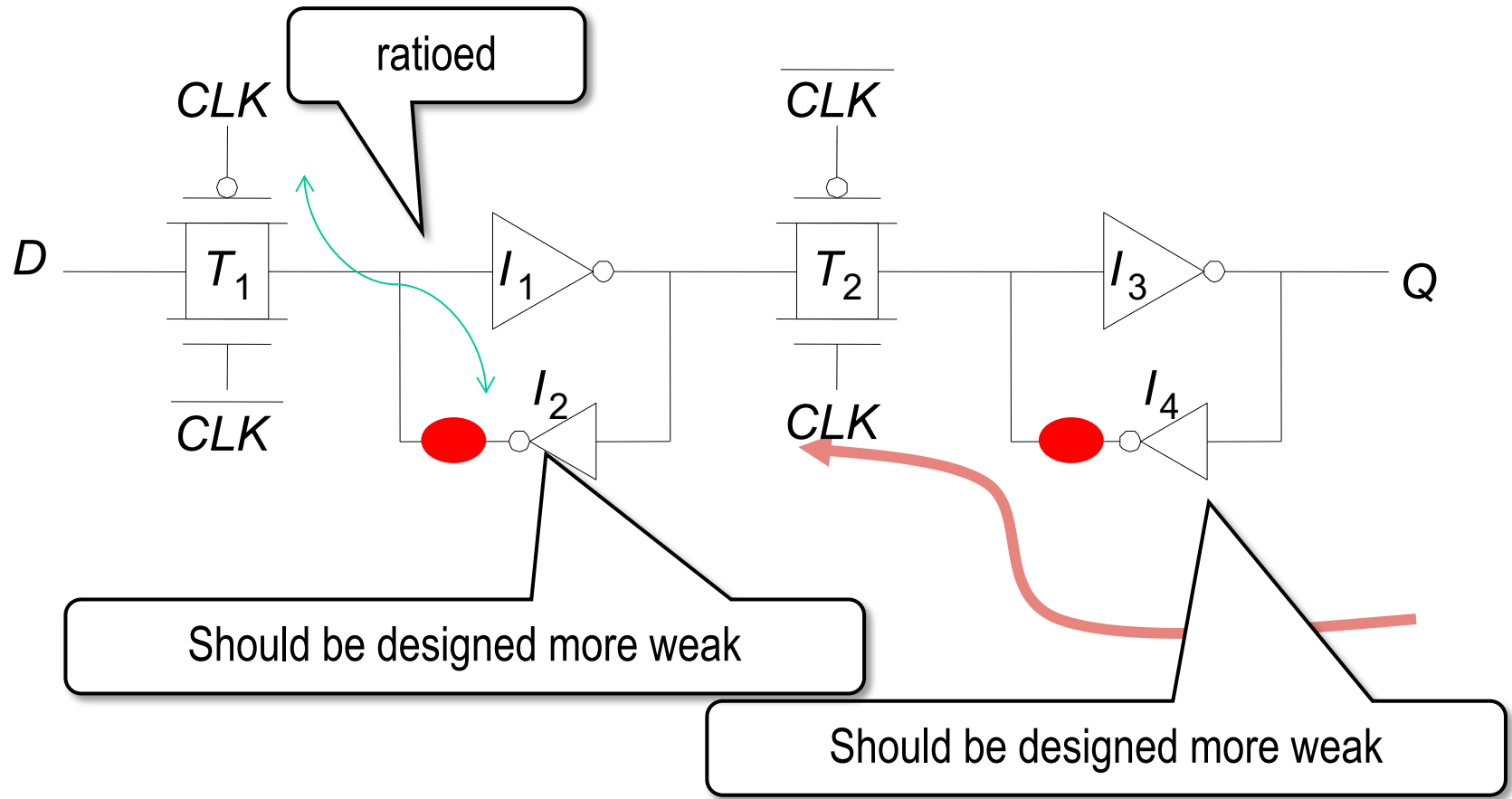
# Reduced Clock Load Master-Slave Register



# Avoiding Clock Overlap

 
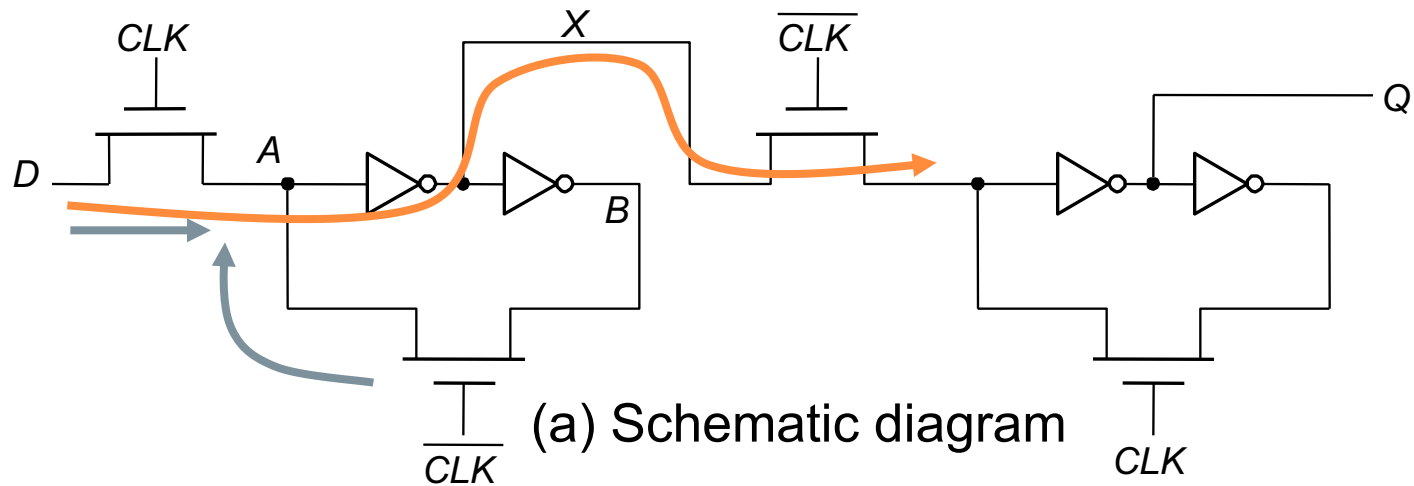


(b) Overlapping clock pairs


  
# *Race and hazard*


*Signal A and Second phase signal, meet with each one at gate G have **Race***



*Result is Error which means **Hazard***
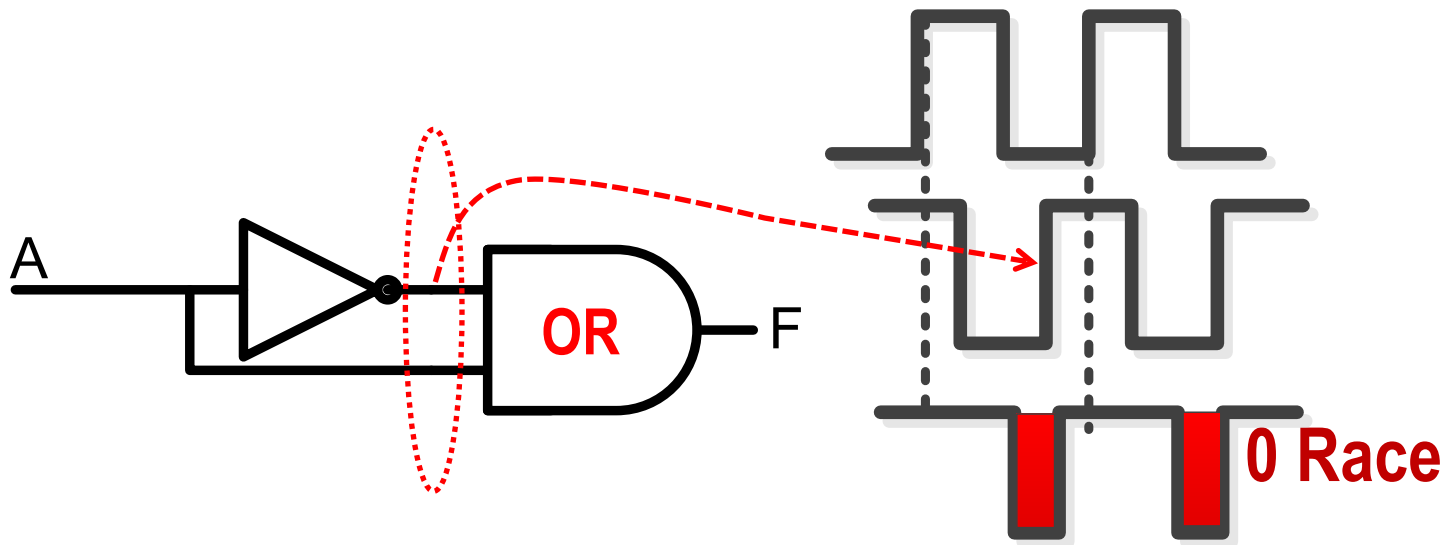
# *Race and hazard*


*Signal A and Second phase signal, meet with each one at gate G have **Race***



*Result is Error which means **Hazard***
 
# Race and hazard

*First phase signal A and Second phase signal P3, meet with each one at gate G4 and have race*





because  $P_3$  after  $A$ , exist a moment of "0" time, hazard happen at  $P_4$

there is a error signal for NOR
  
# Why hazard happen

- **Hazard is driven by race**
- Race condition
  - when at least two input signal change to different direction
  - two changing input come at different time
- **$A$  and  $P_3$  are race signal**



Hazard condition is  $B=0$  let  $A$  and  $P_3$  meet,  $B=1$  not

# Hazard examples

$$P = A + \bar{A}$$

## 0-hazard

Stable state is "1", 0-1, so 0 is unstable hazard state

$$P = A\bar{A}$$

## 1-hazard

Stable state is "0", 1-0, so 1 is unstable hazard state

$$P_1 = AB + \bar{A}C$$

$$P_2 = (A + B)(\bar{A} + C)$$

$$P_3 = \bar{A}B + A\bar{C} + \bar{B}C$$

*When  $B=C=1, P_1=A+\sim A$ , "0" hazard happen*



*When  $B=C=0, P_2=A\sim A$ , "1" hazard happen*

*When  $B=1/C=0, P_3=A+\sim A$ , "0" hazard happen*

*When  $C=1/A=0, P_3=B+\sim B$ , "0" hazard happen*

*When  $A=1/B=0, P_3=C+\sim C$ , "0" hazard happen*

# glitches

 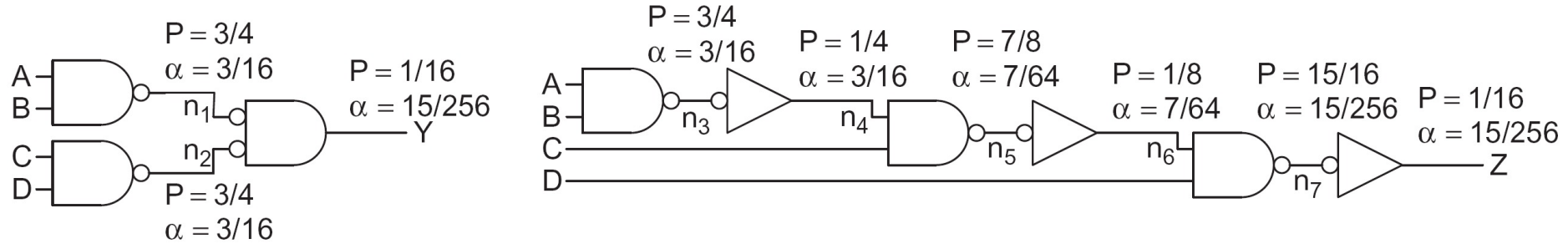


# Design Sequential Logic Circuits


- Introduction
- Timing
- Static Latches and Registers
- ***Dynamic Latches and Registers***



# Dynamic ET Flipflop

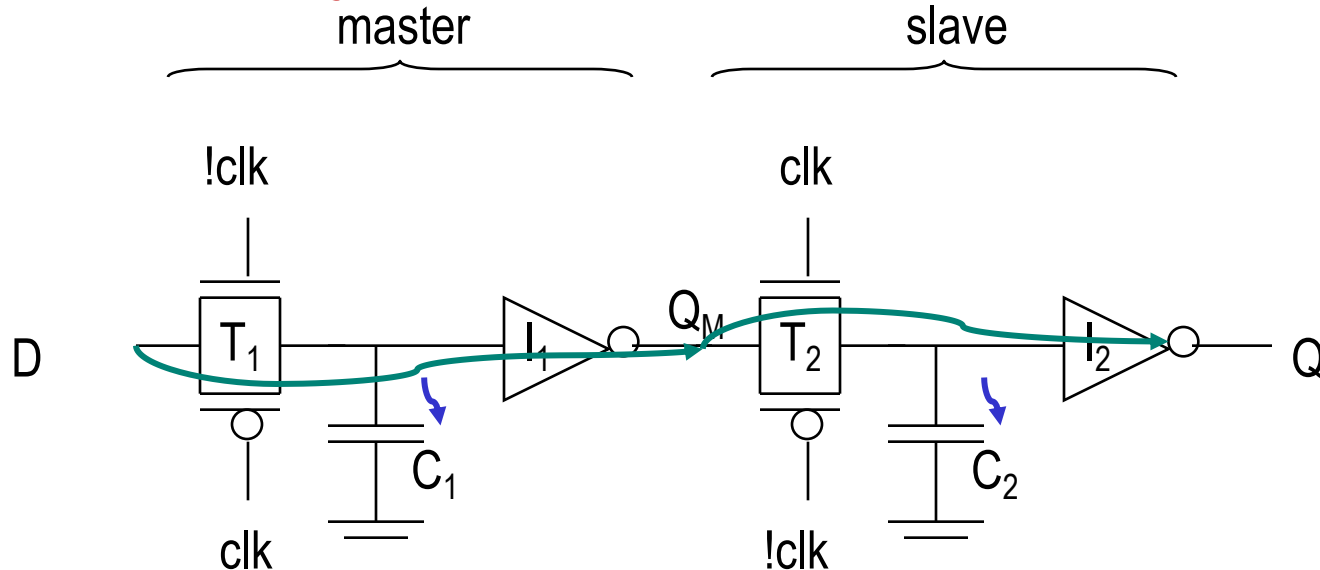

master transparent  
slave hold

 


master hold  
slave transparent

$$\begin{aligned}
 t_{su} &= t_{pd\_tx} \\
 t_{hold} &= \text{zero} \\
 t_{c-q} &= 2 t_{pd\_inv} + t_{pd\_tx}
 \end{aligned}$$




# Dynamic ET FF Race Conditions

 

 0-0 overlap race condition


$$t_{\text{overlap0-0}} < t_{T1} + t_{I1} + t_{T2}$$




1-1 overlap race condition

$$t_{\text{overlap1-1}} < t_{\text{hold}}$$


# Fix 1: Dynamic Two-Phase ET FF

 

master transparent  
slave hold

 

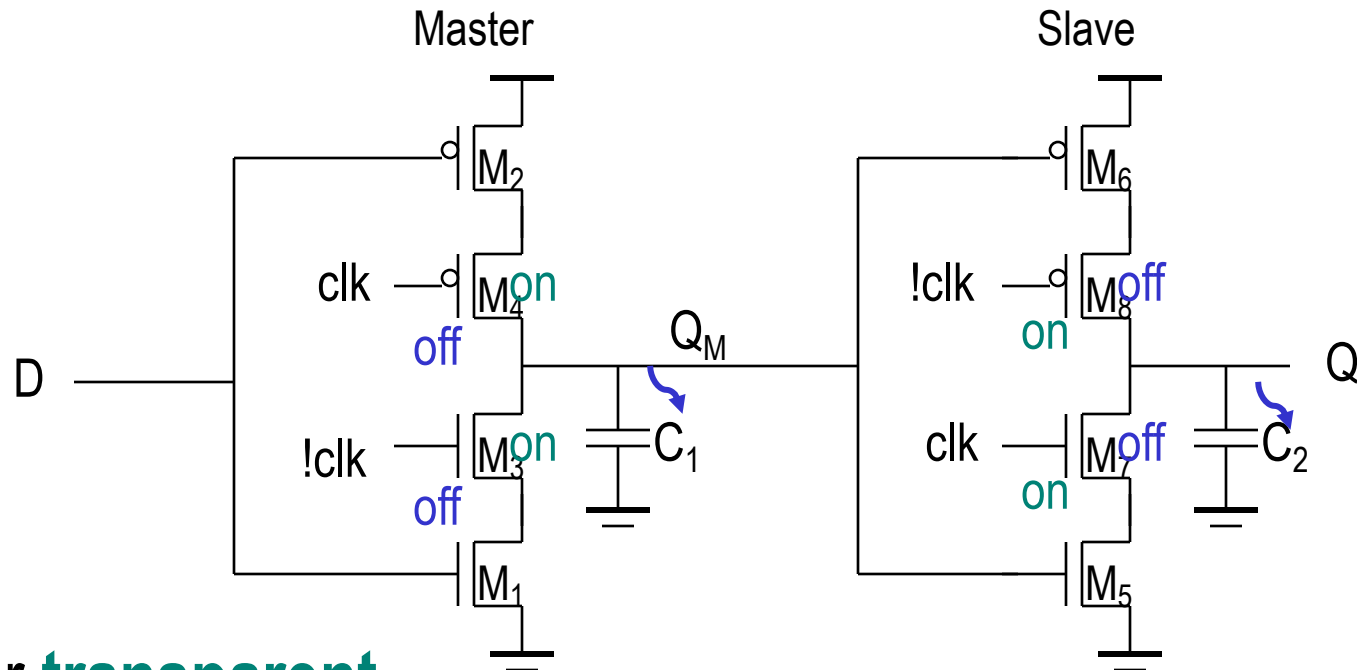
# C<sup>2</sup>MOS (Clocked CMOS) ET Flipflop



master transparent



slave hold

 

master hold

slave transparent


# C<sup>2</sup>MOS FF 0-0 Overlap Case

 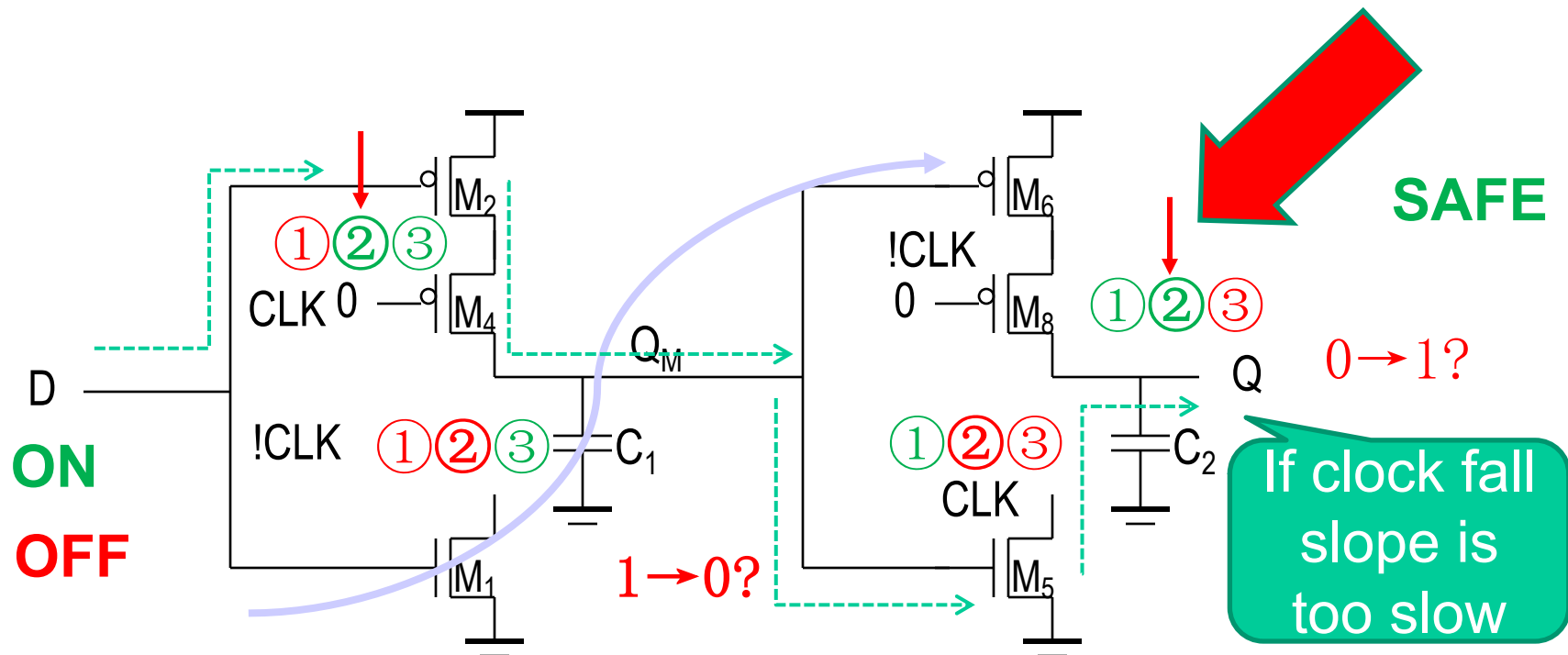

**Hold state...**


***Clock-skew insensitive as long as the rise and fall times of the clock edges are sufficiently small***

# C<sup>2</sup>MOS FF 1-1 Overlap Case

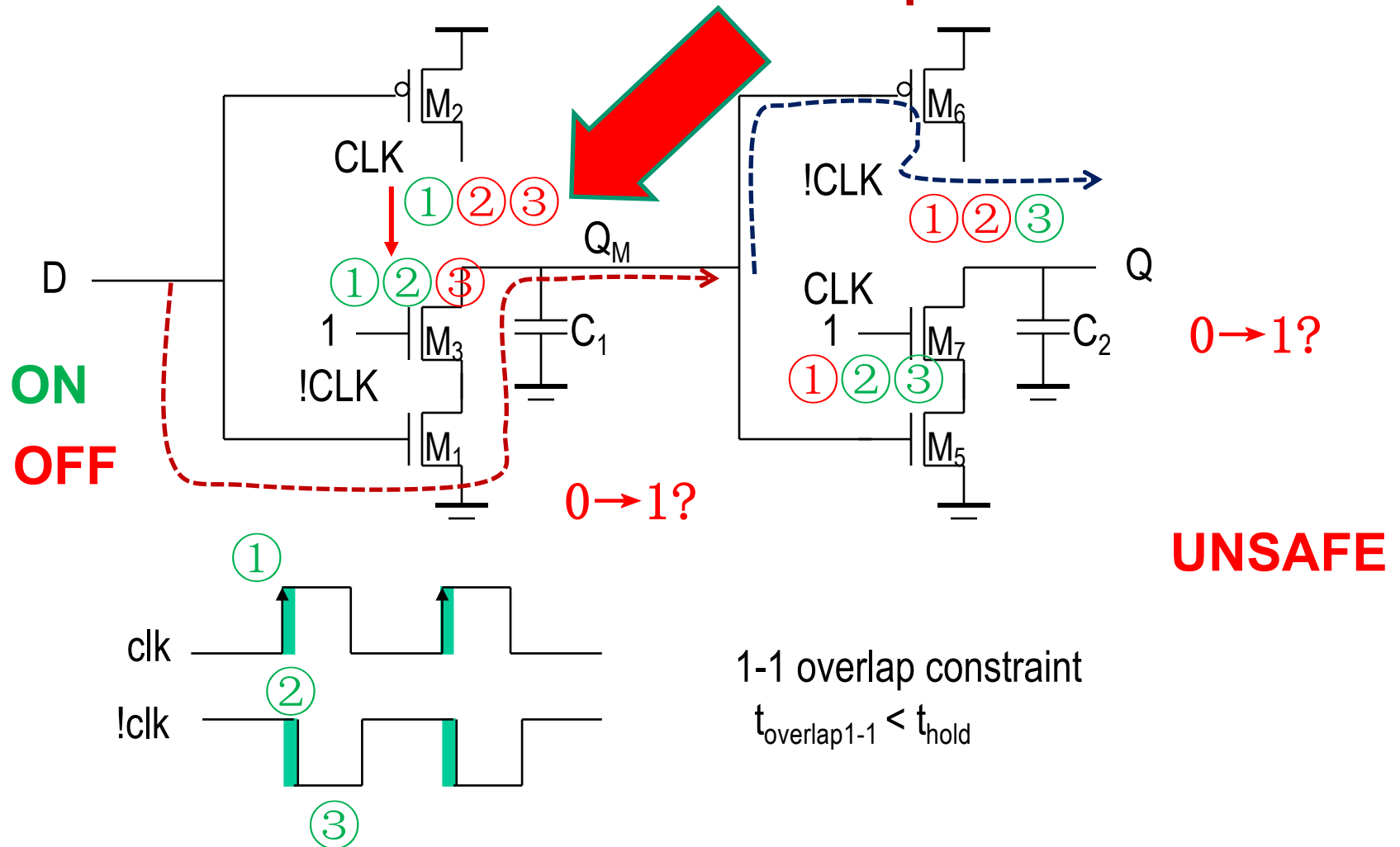

**Setup state...**

# Pipelining using C<sup>2</sup>MOS

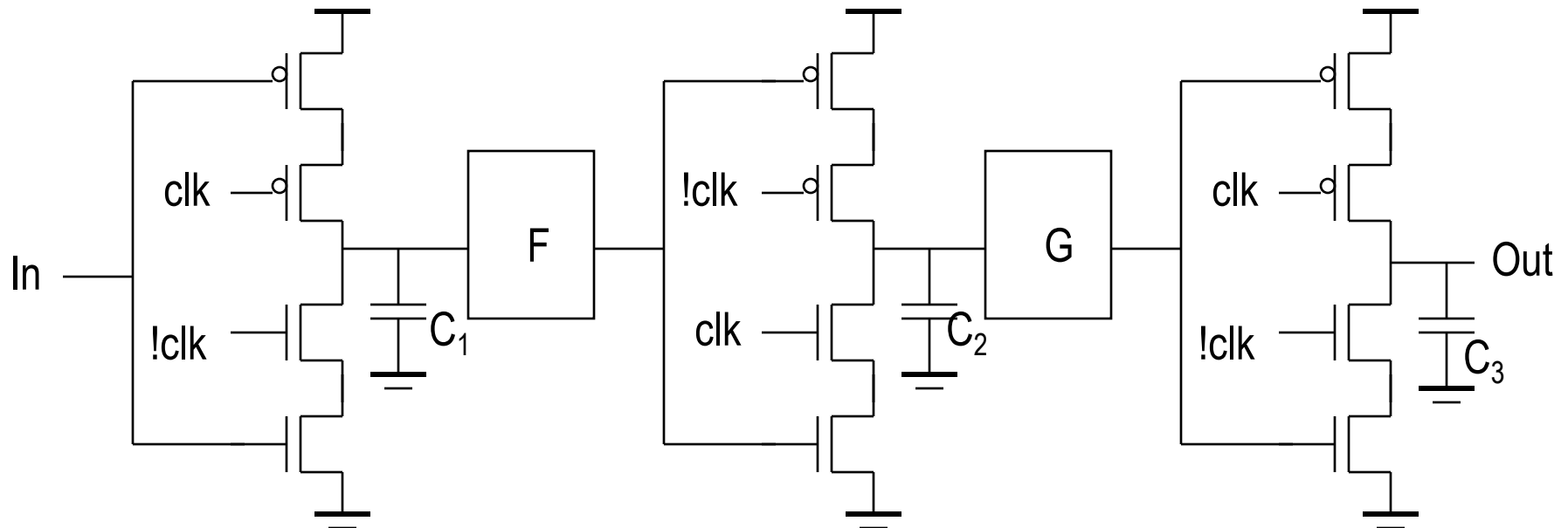


aka NORA (NO RAcE) Logic

What are the constraints on F and G?


# Fix 3: True Single Phase Clocked (TSPC) Latches

Negative Latch

 

*hold* when  $clk = 1$   
*transparent* when  $clk = 0$


Positive Latch

 

*transparent* when  $clk = 1$   
*hold* when  $clk = 0$

# Traditional Domino Circuits

- Ping-pang approach for overlapping the precharge time

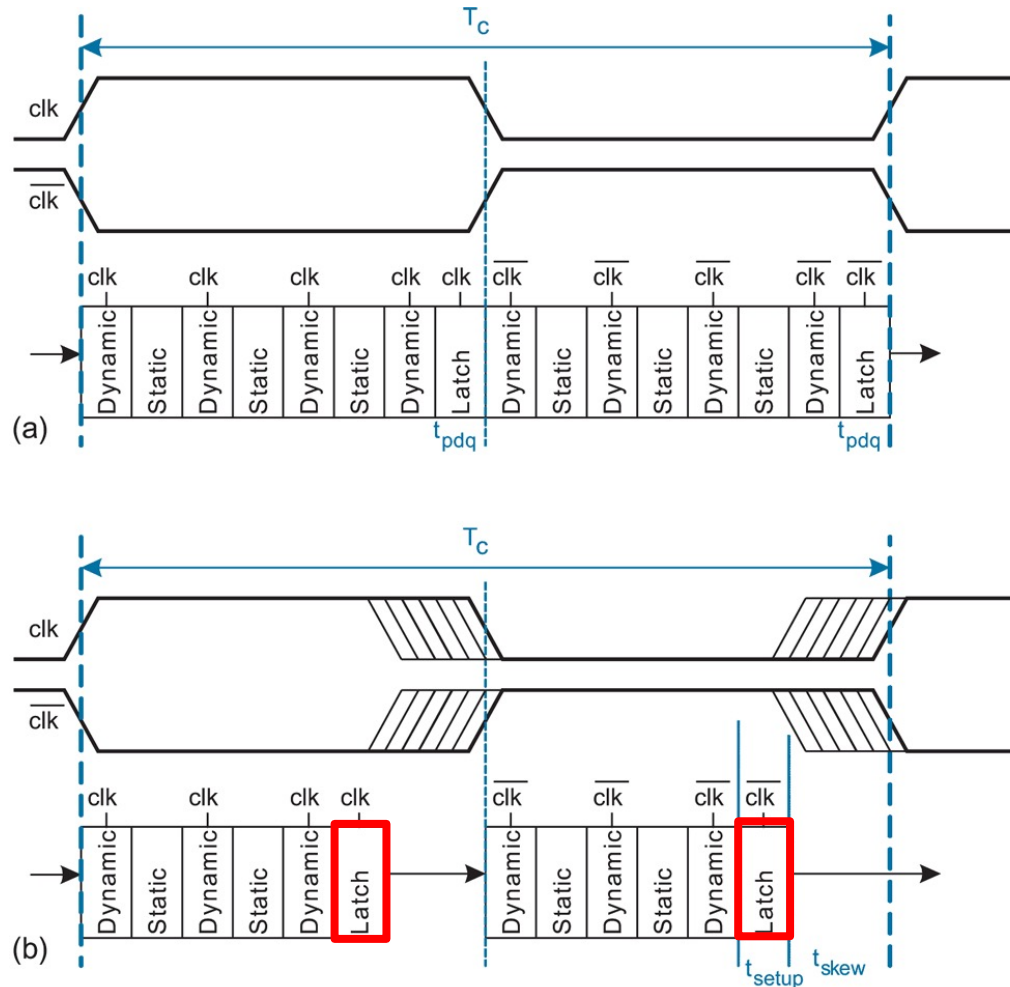


**FIG 7.43** Traditional domino circuits




# Skew-tolerant Domino Circuits

- Latch function
  - Prevent nonmonotonic signals from entering the next domino gate while it evaluates
  - Hold the results of the half-cycle while it precharges and the next half-cycle evaluates

 

**FIG 7.44** Eliminating latches in skew-tolerant domino circuits

 

**FIG 7.45** Full keeper