

review

Exam contents



- Combination circuit logic
- wire
- Datapath
- Sequential circuit Logic

Exam contents


- **Combination circuit logic**
- wire
- Datapath
- Sequential circuit Logic

Combination logic.

- CMOS logic Properties

  


Sizing has different options

 

$$OUT = \overline{D + A \cdot (B + C)}$$

Delay Dependence on **Input Patterns**

Shared cap. **discharging**

 

Shared cap. **charging**

Input Data Pattern	Delay (psec)
A=B=0→1	69(max)
A=1, B=0→1	62
A= 0→1, B=1	50
A=B=1→0	35(min)
A=1, B=1→0	76
A= 1→0, B=1	57

NMOS = 0.5 μ m/0.25 μ m
 PMOS = 0.75 μ m/0.25 μ m
 C_L = 100 fF

Modified formula

$$t_p = t_{par} + t_{ext} = \ln 2. (C_{par} + C_{ext}) R_{par}$$

$$= \ln 2. R_{inv} C_{int} \left(\frac{C_{par}}{C_{int}} + \frac{C_g}{C_{int}} \frac{C_{ext}}{C_g} \right)$$

$$= t_{p0} \left(\frac{C_{par}}{C_{int}} + \frac{C_g}{C_{int}} \frac{C_{ext}}{C_g} \right)$$


$$= t_{p0} \left(\frac{C_{par}}{\boxed{C_{int}}} + \frac{C_g}{\boxed{\gamma C_{ginv}}} \frac{C_{ext}}{C_g} \right)$$

$$= t_{p0} \left(p + \frac{gf}{\gamma} \right)$$

$$\boxed{C_{ginv} \mid R_{par} = R_{inv}}$$

 
Example: 3-stage path

- Select gate sizes x and y for least delay from A to B




Asymmetric Gates

 - Asymmetric gates favor one input over another
- Ex: suppose input A of a NAND gate is most critical
 - Use smaller transistor on A (less capacitance)
 - Boost size of noncritical input
 - So total resistance is same



 - $g_A = 10/9$
- $g_B = 2$
- $g_{\text{total}} = g_A + g_B = 28/9$
- Asymmetric gate approaches $g = 1$ on critical input
- But total logical effort goes up



the special Path Optimization




Catalog of Skewed Gates

Inverter




NAND2

NOR2




unskewed

   

HI-skew

   



LO-skew

   


Complementary Pass Transistor Logic




(a)

  

AND/NAND

 


OR/NOR

 

EXOR/NEXOR


(b)

Solution 1: Level Restoring Transistor

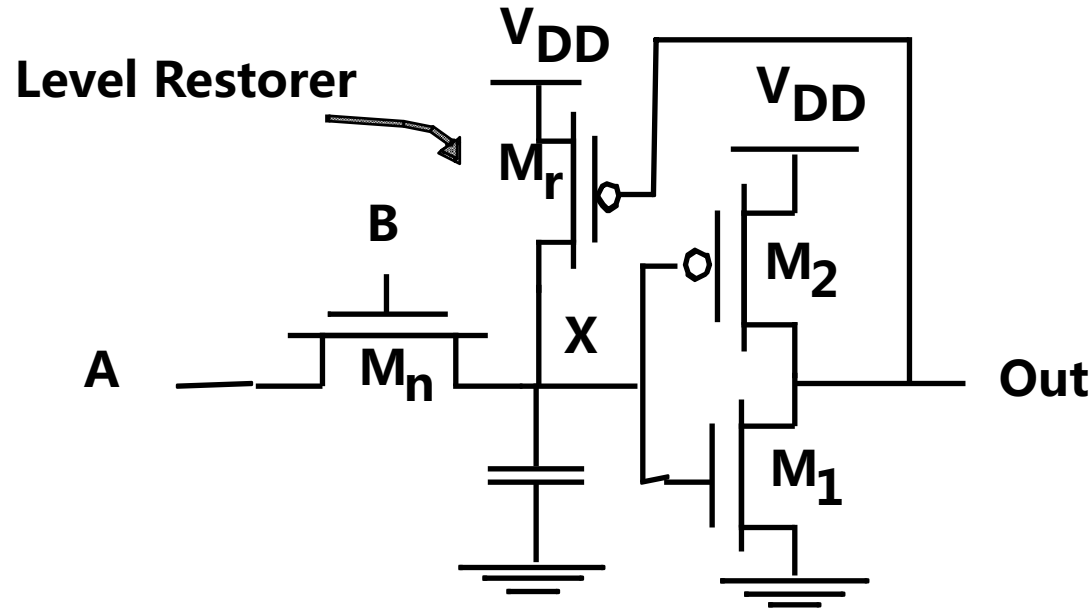


- Advantage: Full Swing
- Restorer adds capacitance, takes away pull down current at X
- Ratio problem

Transmission Gate XOR

 


Dynamic Gate

 

Two phase operation

Precharge ($Clk = 0$)


Evaluate ($Clk = 1$)

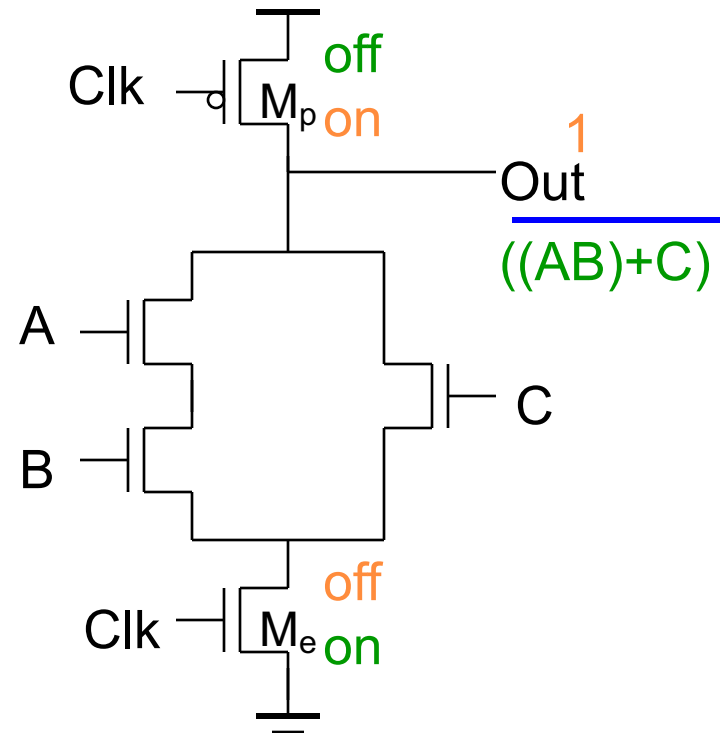


Logical Effort

unfooted


Inverter

 




NAND2

 

NOR2

 

footed

   

Monotonicity



- Dynamic gates require *monotonically rising* inputs during evaluation

– 0 -> 0

– 0 -> 1


– 1 -> 1

– *But not 1 -> 0*

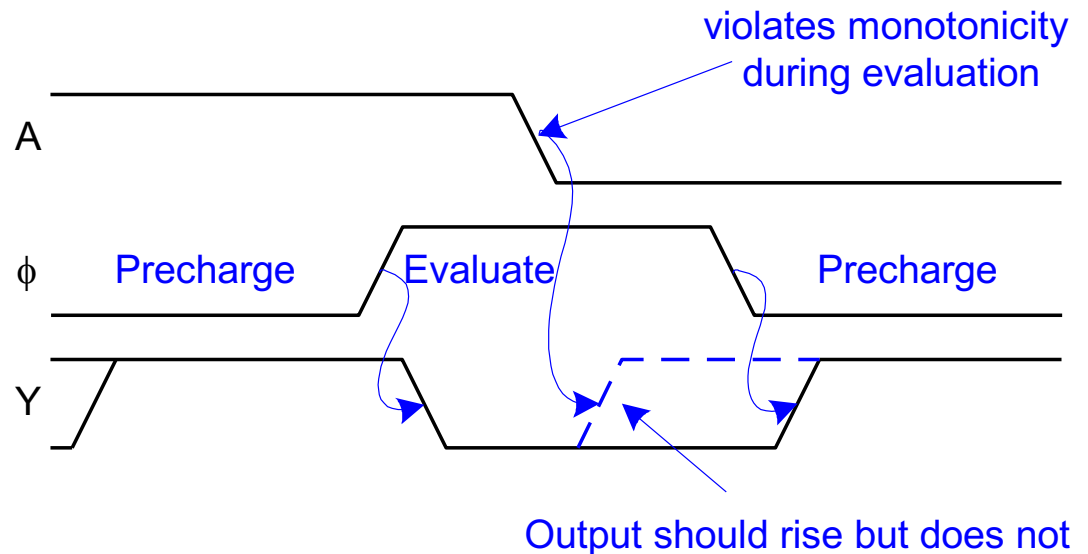 


Monotonicity Woes

 - But dynamic gates produce monotonically falling outputs during evaluation
- Illegal for one dynamic gate to drive another!






$A = 1$

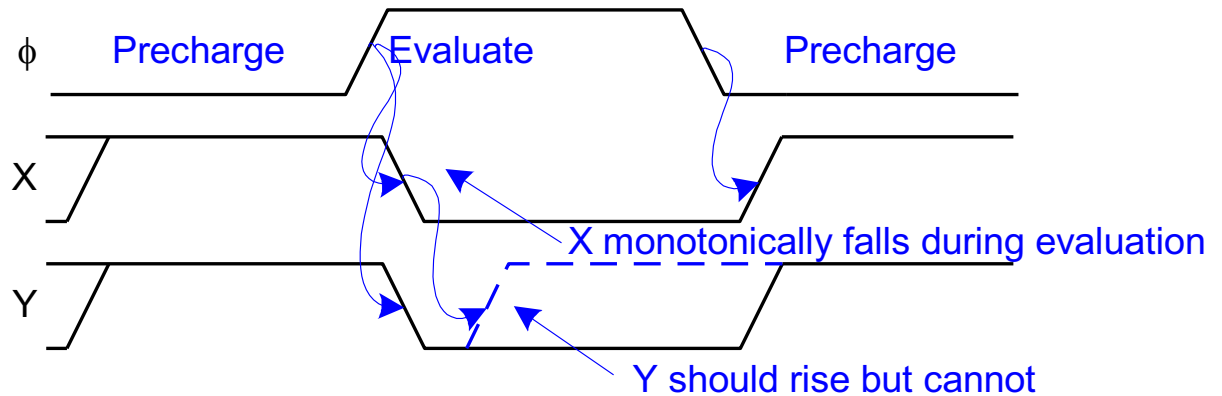


Domino Gates

  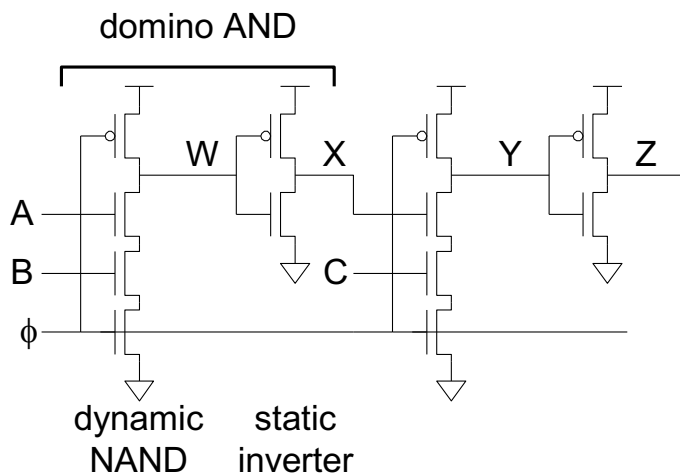- Follow dynamic stage with inverting static gate
 - Dynamic / static pair is called domino gate
 - Produces monotonic outputs




 Issues in Dynamic Design 1: Charge Leakage



Dominant component is subthreshold current

 Issues in Dynamic Design 2: Charge Sharing





Charge stored originally on C_L is redistributed (shared) over C_L and C_A leading to reduced robustness

Could we move it to there?

Exam contents

- Combination circuit logic
- **wire**
- Datapath
- Sequential circuit Logic

Lumped RC Model

  


**Pessimistic
approximation**

time const = RC

Elmore Delay of RC-Network

 - *Does not have any resistive loops*
- *All capacitances are between a node and a ground*
- *Have a single input node*



$$\tau_{Di} = R_1 C_1 + R_1 C_2 + (R_1 + R_3) C_3 + (R_1 + R_3) C_4 + (R_1 + R_3 + R_i) C_i$$

traverse all C 's


$$\tau_{Di} = \sum_{k=1}^N \boxed{C_k} R_{ik}$$

$$R_{ik} = \sum R_j \quad \text{for } R_j \in \boxed{\text{path}(r \rightarrow i) \cap \text{path}(r \rightarrow k)}$$

shared path

Delay Elmore Delay – Another Solution

Search all C

 

R_1 drives C_1, C_2, C_3, C_4, C_5
 R_3 drives C_3, C_4, C_5
 R_5 drives C_5

$$\tau_{D5} = R_1 C_1 + R_1 C_2 + (R_1 + R_3) C_3 + (R_1 + R_3) C_4 + (R_1 + R_3 + R_5) C_5$$




$$\tau_{D5} = R_1 (C_1 + C_2 + C_3 + C_4 + C_5) + R_3 (C_3 + C_4 + C_5) + R_5 C_5$$



downstream from the root

$$\tau_{s \rightarrow t} = \sum_{R_k \text{ along path } s \rightarrow t} R_k \text{ (sum of } C_i \text{ driven by } R_k \text{)}$$


Which model is the fastest one

 

  
$$\sum_{i=1}^N (R_s + \frac{i}{N} R) \frac{C}{N} = R_s C + \frac{N(N+1)}{2N} R \frac{C}{N} = R_s C + \frac{(N+1)}{2N} RC$$


 
$$R_s \frac{C}{2N} + \sum_{i=1}^{N-1} (R_s + \frac{i}{N} R) \frac{C}{N} + (R_s + \frac{N}{N} R) \frac{C}{2N} = R_s C + \frac{N}{2N} RC$$



Which model is the fastest one

 


$$\sum_{i=1}^N \left(R_s + \frac{1}{2N} R + \frac{i-1}{N} R \right) \frac{C}{N} = R_s C + \frac{RC}{2N} + \frac{N(N-1)}{2N} R \frac{C}{N} = R_s C + \frac{N}{2N} RC$$

Exam contents

- Combination circuit logic
- wire
- **Datapath**
- Sequential circuit Logic

Inversion Property

 

$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$


$$\bar{C}_o(A, B, C_i) = C_o(\bar{A}, \bar{B}, \bar{C}_i)$$

A	B	C	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Mirror Adder-Stick Diagram

$$C_o = AB + BC_i + AC_i$$
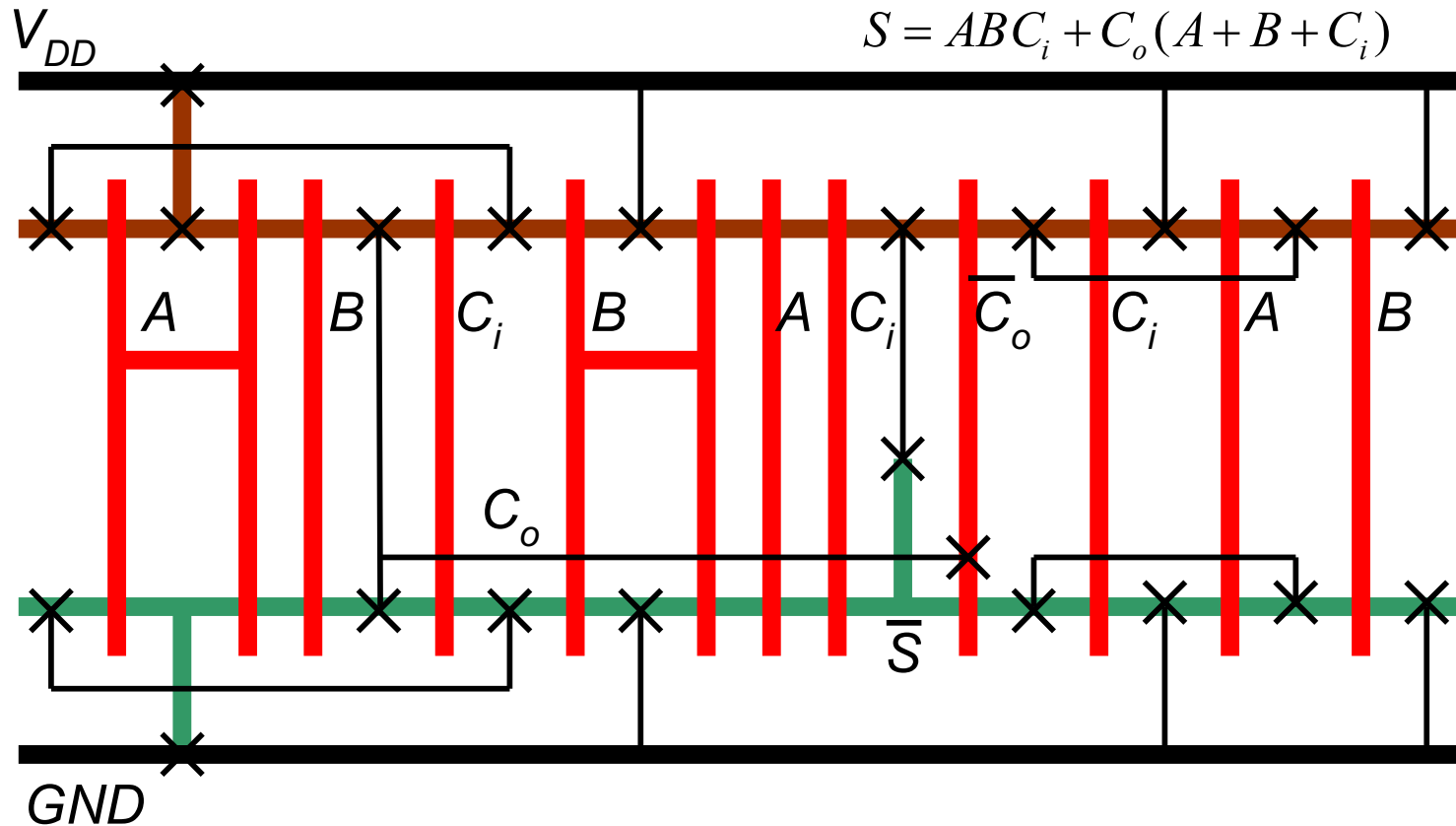
$$S = ABC_i + \overline{C_o}(A + B + C_i)$$



Single-Bit Addition

Half Adder

$$S = A \oplus B$$

$$C_{out} = AB$$


A	B	C _{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C + ABC$$

$$= A \oplus B \oplus C = P \oplus C$$

$$C_{out} = AB + (A + B)C$$

 
$$= \overline{\overline{A}\overline{B}} + \overline{(\overline{A} + \overline{B})\overline{C}} = MAJ(A, B, C)$$



Full Adder

$$S = A \oplus B \oplus C$$

$$C_{out} = MAJ(A, B, C)$$

 

A	B	C	C _{out}	S	P	G
0	0	0	0	0	0	0
0	0	1	0	1	0	0
0	1	0	0	1	1	0
0	1	1	1	0	1	0
1	0	0	0	1	1	0
1	0	1	1	0	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	1

Delete/Kill

propagate

generate

Full Adder Design IV

$$S = A \oplus B \oplus C = P \oplus C$$

$$C_{out} = AB + (A \oplus B)C = AAB + A\bar{A}\bar{B} + (A \oplus B)C = A\bar{P} + PC$$

$$\overline{C_{out}} = (\bar{A} + P)(\bar{P} + \bar{C}) = \bar{A}\bar{P} + \bar{A}\bar{C} + P\bar{C} = \bar{A}\bar{P} + \bar{A}\bar{C}\bar{P} + \bar{A}\bar{C}P + P\bar{C} = \bar{A}\bar{P} + P\bar{C}$$


 
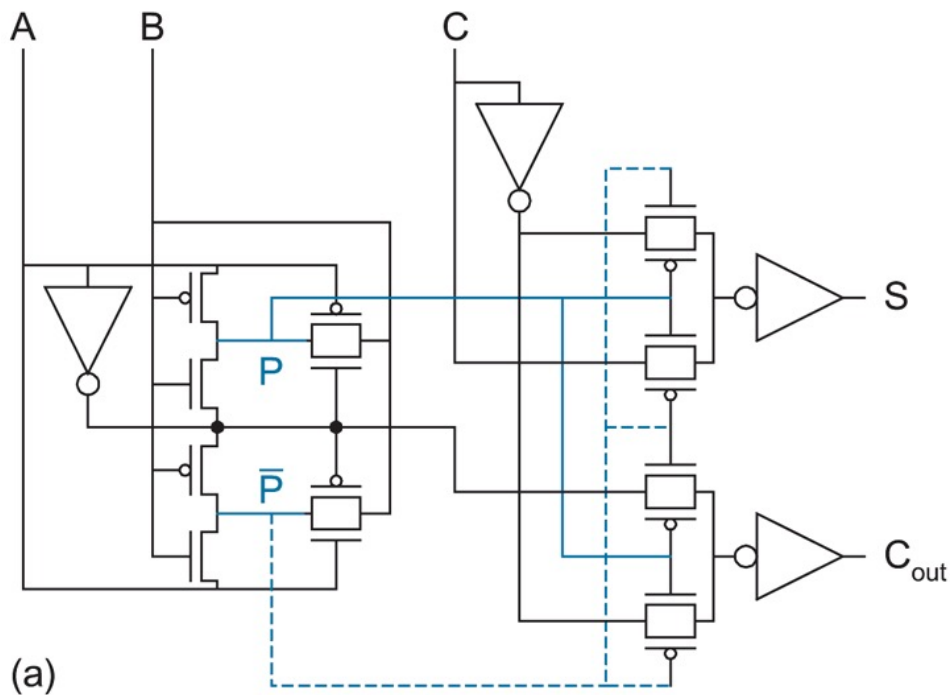


FIG 10.6 Transmission gate full adder

Carry-Skip PG Diagram

 

$$G_{4:0} = G_{4:1} + P_{4:1}G_{0:0}$$

$$G_{8:0} = G_{8:5} + P_{8:5}G_{4:0}$$


$$G_{12:0} = G_{12:0} + P_{12:9}G_{8:0}$$

$$G_{16:0} = G_{16:13} + P_{16:13}G_{12:0}$$

$$t_{\text{skip}} = t_{pg} + [2(n-1) + (k-1)]t_{AO} + t_{\text{xor}}$$

Carry-Select Adder

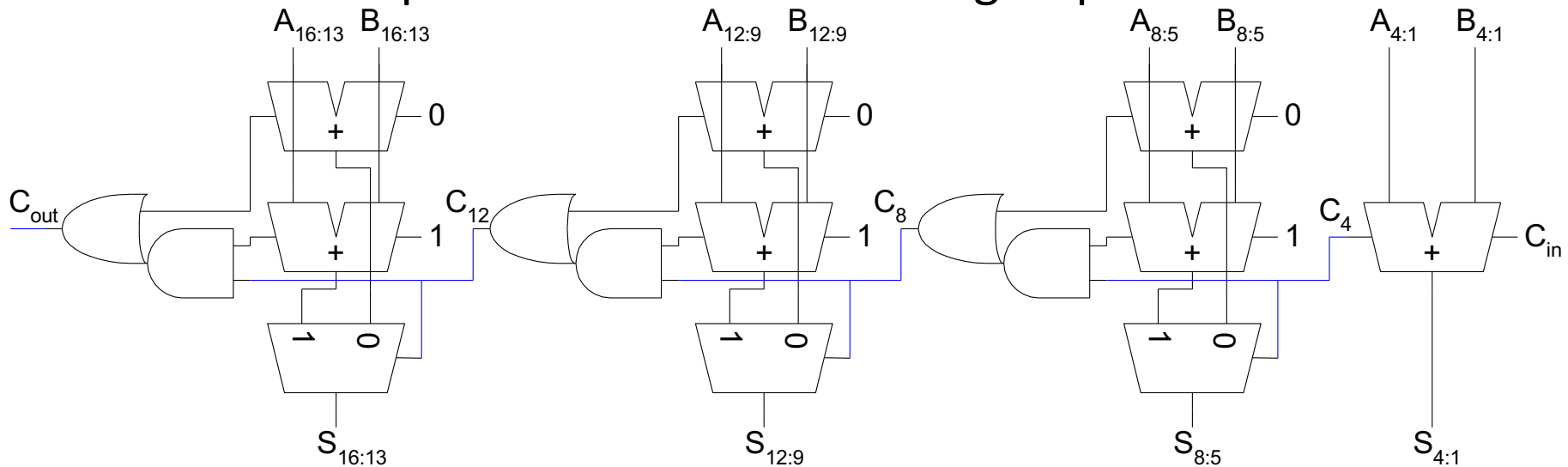
- Trick for critical paths dependent on late input X
 - Precompute two possible outputs for $X = 0, 1$
 - Select proper output when X arrives
- Carry-select adder precomputes n-bit sums
 - For both possible carries into n-bit group



$$t_{select} = t_{pg} + [n + (k - 2)]t_{AO} + t_{mux}$$


Han-Carlson(B+K tree)

Kogge Stone — — — Brent Kung

 


Ladner-Fischer(S+B)

Sklansky — — — — Brent Kung

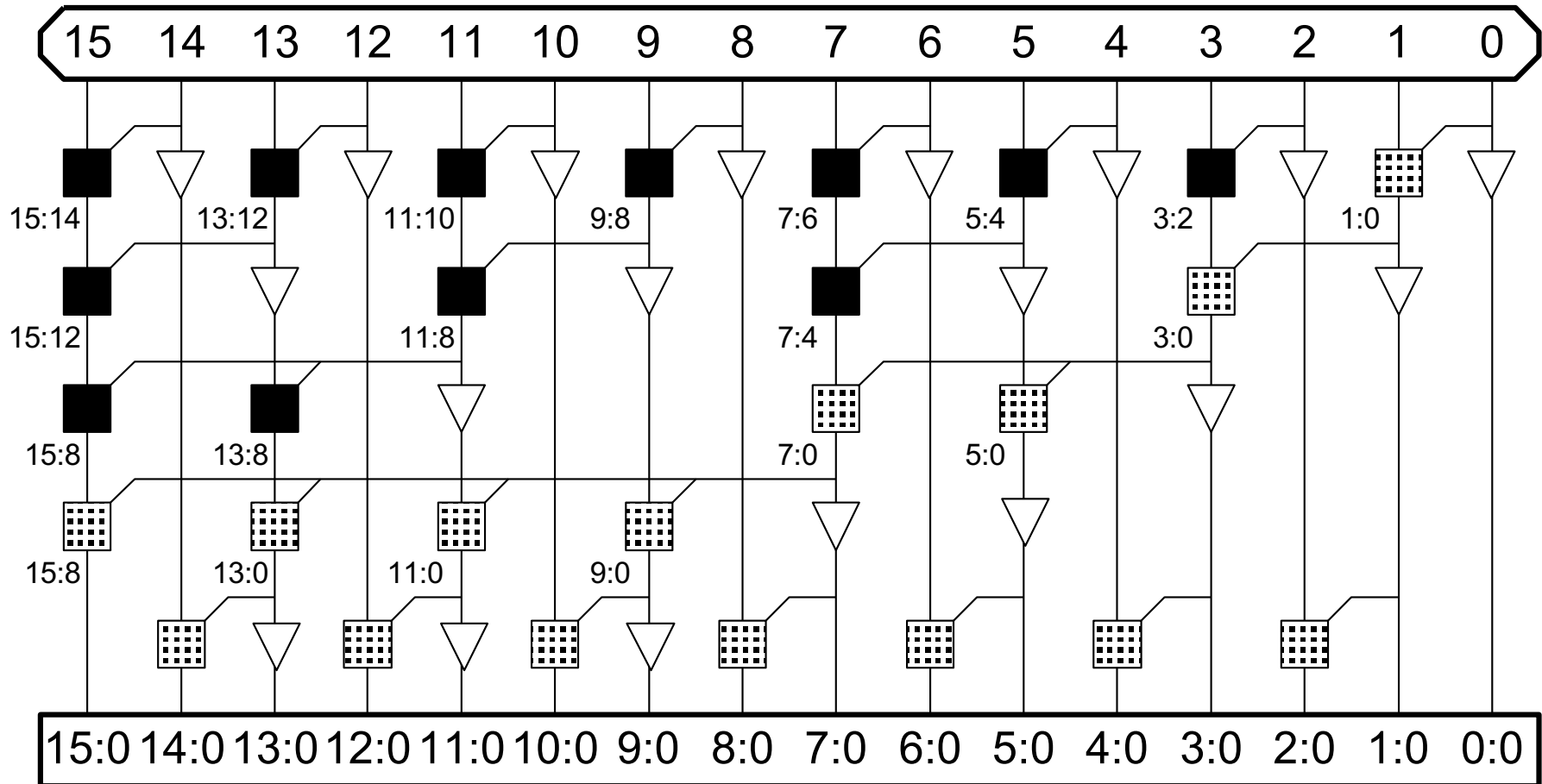

Knowles [1, 1, 1, 2](S+K)

Kogge Stone — — — — *Sklansky*


 


Exam contents





- Combination circuit logic
- wire
- Datapath
- **Sequential circuit Logic**

Timing Diagrams

Contamination and Propagation Delays

  

t_{pd}	Logic Prop. Delay
t_{cd}	Logic Cont. Delay
t_{pcq}	Latch/Flop Clk-Q Prop Delay
t_{ccq}	Latch/Flop Clk-Q Cont. Delay
t_{pdq}	Latch D-Q Prop Delay
t_{pcq}	Latch D-Q Cont. Delay
t_{setup}	Latch/Flop Setup Time
t_{hold}	Latch/Flop Hold Time

    

Clock skew about FF *negative skew*

$$t_{pdq} \leq T_c - (t_{pcq} + t_{setup} + t_{skew})$$


Positive skew for better condition

Large is better !

Ex. $t_{pcq}=20ps, t_{setup}=30ps, T_c=300ps, t_{skew}=50ps$


$t_{pdq} \leq 300-20-30=250$, $t_{pdq}=240$ is OK

 Including skew delay, $t_{pdq} \leq 300-20-30-50=200ps$, $t_{pdq}=240$ is not OK!



Clock skew about FF

Small is better !

 

$$t_{cd} \geq t_{hold} - t_{ccq} + t_{skew}$$

Positive skew for worse condition

Ex: $t_{cd}=20ps, t_{hold}=20ps, t_{ccq}=2ps, t_{skew}=5ps$

$t_{cd} \geq 20-2=18, t_{cd}=20$ is OK!

Including skew delay, $t_{cd} \geq 20-2+5=23, 20$ is Not OK

