

Digital Integrated Circuits

***Designing Combinational
Logic Circuits***

Fuyuzhuo

Dynamic Logic

Dynamic logic outline


- *Dynamic logic principle*
- Dynamic logic properties
- Dynamic logic design issues
- Dynamic logic cascade solution

Static or ***Dynamic***



A first glance of dynamic logic

 
- Basic components
 - PDN, just like CMOS and pseudo-NMOS
 - Clock control transistors ,
separate circuit to two phases
- Dynamic logic's two phases
 - precharge
 - evaluation



Dynamic CMOS

- **Static** circuits at every point in time (except when switching) the output is connected to either GND or V_{DD} via a low resistance path.
 - fan-in of n requires $2n$ (n N-type + n P-type) devices
- **Dynamic** circuits rely on the temporary storage of signal values on the capacitance of high impedance nodes.
 - requires on $n + 2$ ($n+1$ N-type + 1 P-type) transistors


Dynamic Gate

 

Two phase operation

Precharge ($Clk = 0$)

Evaluate ($Clk = 1$)

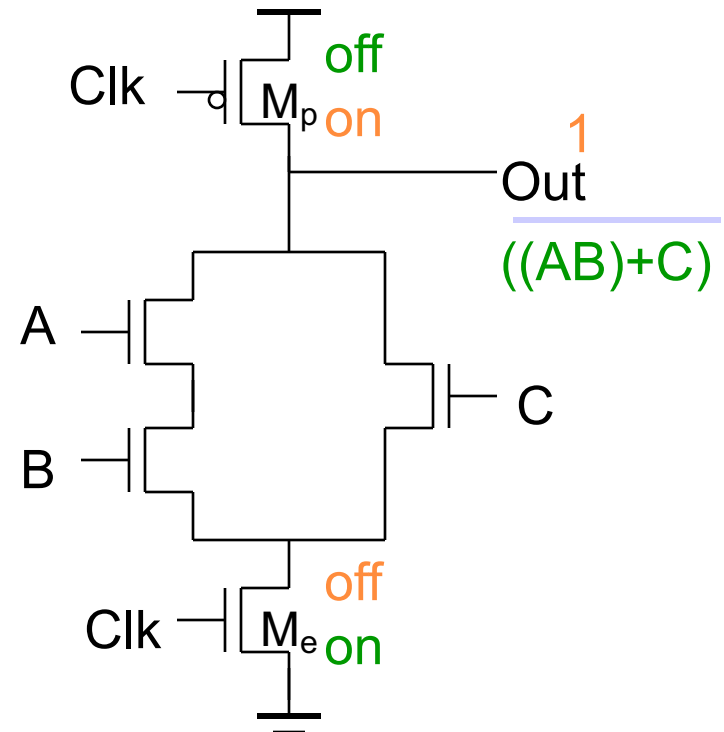


Conditions on Output

- Once the output of a dynamic gate is discharged, it cannot be charged again until the next precharge operation
- Inputs to the gate can make **at most** one transition during evaluation.
- Output can be in the high impedance state during and after evaluation (PDN off), state is stored on C_L


Dynamic Logic

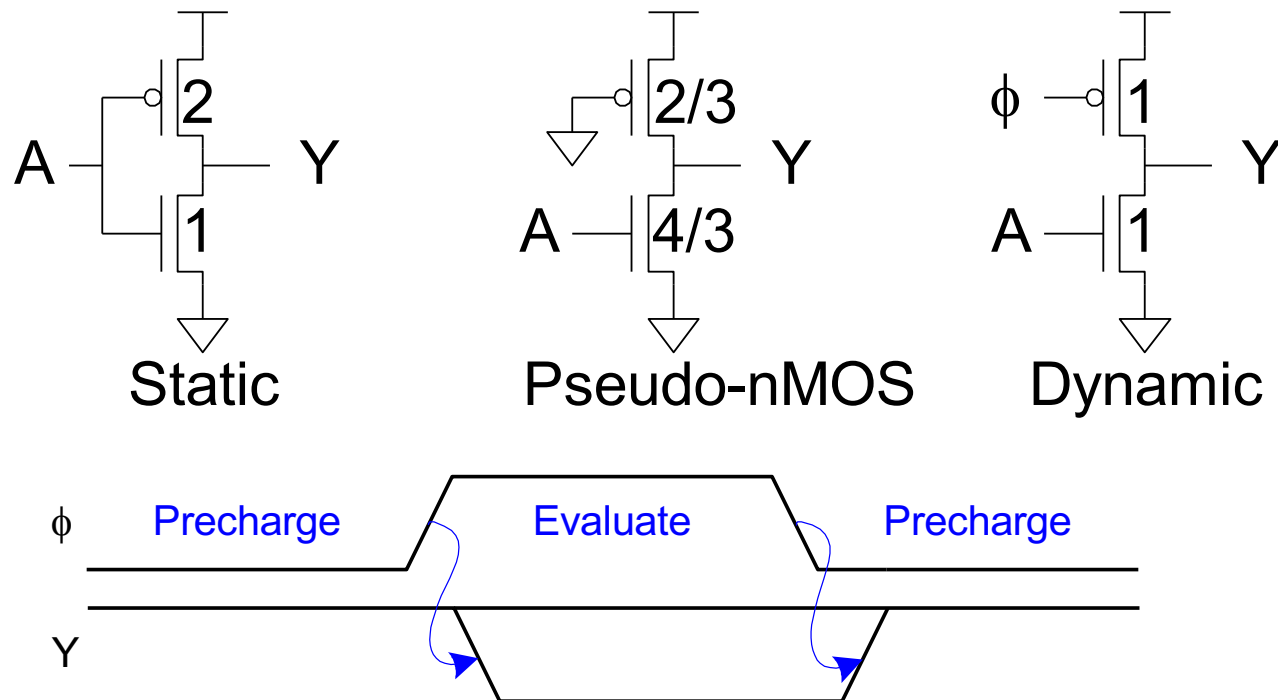- *Dynamic* gates uses a clocked pMOS pullup
- Two modes: *precharge* and *evaluate*



The Foot

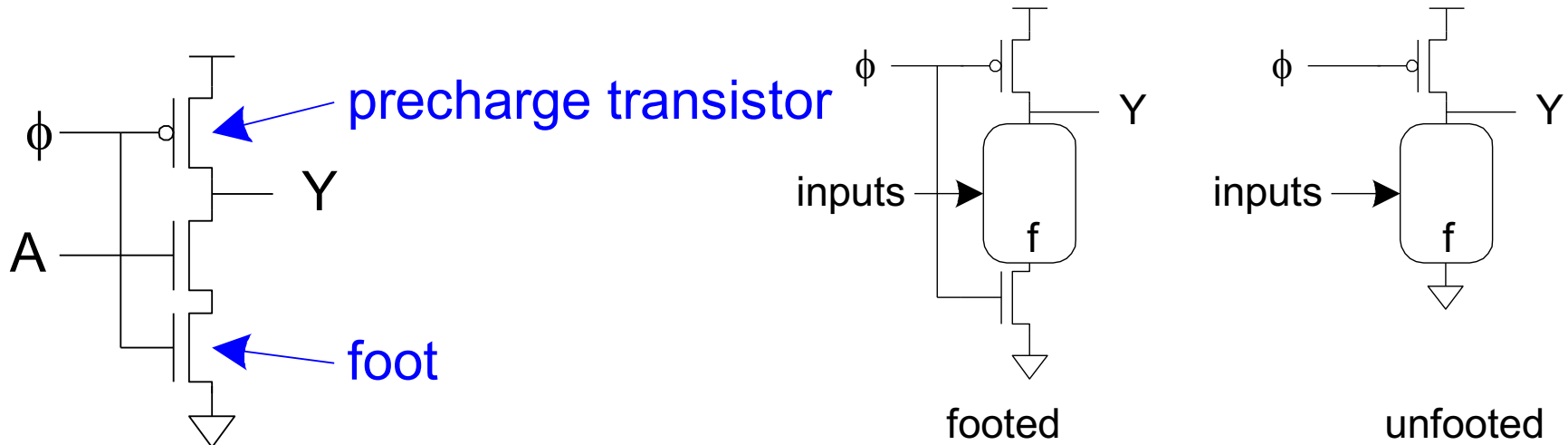
- What if pulldown network is ON during precharge?
- Use series evaluation transistor to prevent fight.




Logical Effort

unfooted


Inverter

 




NAND2

 

NOR2

 


footed

   


Logical Effort

unfooted


Inverter

 




NAND2

 

NOR2


 


footed

   



Monotonicity

  - Dynamic gates require *monotonically rising* inputs during evaluation
 - 0 -> 0
 - 0 -> 1
 - 1 -> 1
 - But not 1 -> 0**





Monotonicity Woes

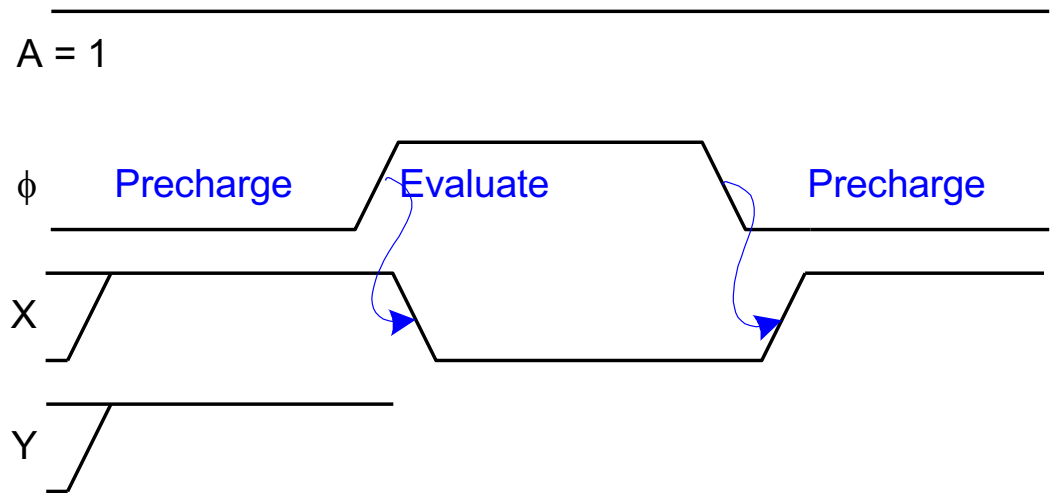 - But dynamic gates produce monotonically falling outputs during evaluation
- Illegal for one dynamic gate to drive another!



Monotonicity Woes

  - But dynamic gates produce monotonically falling outputs during evaluation
- Illegal for one dynamic gate to drive another!



Dynamic logic outline

- Dynamic logic principle
- ***Dynamic logic properties***
- Dynamic logic design issues
- Dynamic logic cascade solution



Properties of Dynamic Gates

- ✓ Logic function is implemented by the PDN only
 - number of transistors is $N + 2$ (versus $2N$ for static complementary CMOS)
- ✓ Full swing outputs ($V_{OL} = \text{GND}$ and $V_{OH} = V_{DD}$)
- ✓ Non-ratioed
 - sizing of the devices does not affect the logic levels
- ✓ Faster switching speeds
 - reduced load capacitance due to **lower input** capacitance (C_{in})
 - reduced load capacitance due to smaller output loading (C_{out})

Properties of Dynamic Gates

- # Overall power dissipation usually **higher** than static CMOS
 - no static current path ever exists between V_{DD} and GND (including P_{sc})
 - No glitching
 - *higher transition probabilities*
 - *extra load on Clk*
- # PDN starts to work when the input signals exceed V_{Tn}
 - V_M , V_{IH} and V_{IL} equal to V_{Tn}
 - low noise margin (NM_L)
- # Needs a precharge/evaluate clock


A 4-NAND dynamic logic VTC

  

A 4-NAND dynamic logic V_{TC}

面积	静态 电流	晶体管 数目	V_{OH}	V_{OL}	V_M	NM_H	NM_L	t_{pHL}	t_{pLH}	t_p
212	0	6	5V	0V	0.75V	4.25V	0.75V	0.74nsec	0	0.37nsec

 
- Small load capacity
- Asymmetry of noise margin
- Small delay
- Fewer transistors



Dynamic logic outline


- Dynamic logic principle
- Dynamic logic properties
- ***Dynamic logic design issues***
 - ***Charge-leakage***
 - Charge-sharing
 - Backgate Coupling
 - Clock feedthrough
- Dynamic logic cascade solution

 Issues in Dynamic Design 1: Charge Leakage



Dominant component is subthreshold current

Solution to Charge Leakage

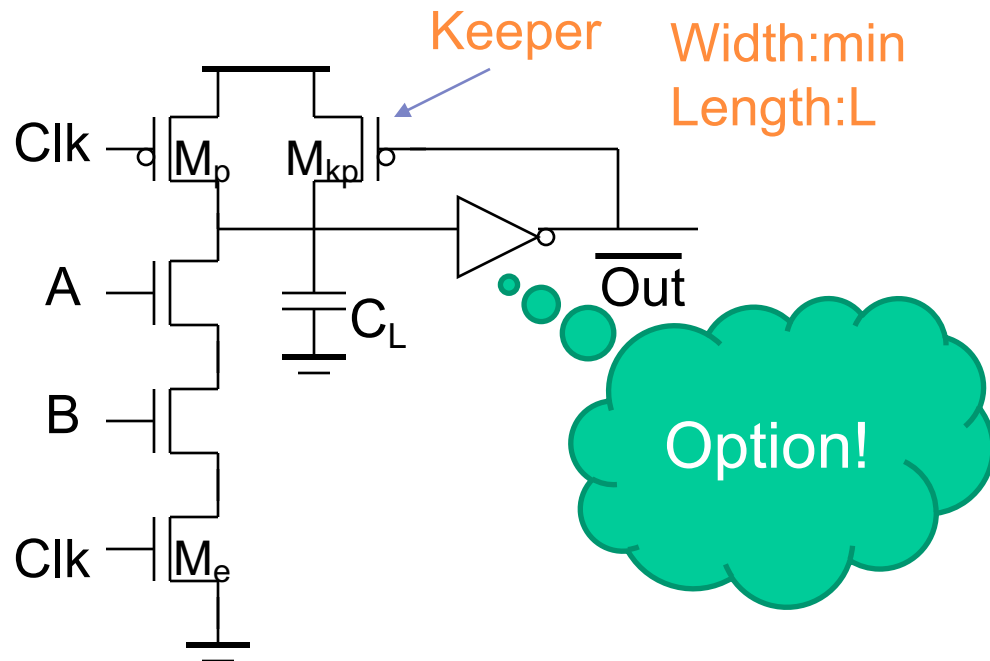


Same approach as level restorer for pass-transistor logic

Dynamic logic outline

- Dynamic logic principle
- Dynamic logic properties
- ***Dynamic logic design issues***
 - Charge-leakage
 - ***Charge-sharing***
 - Backgate Coupling
 - Clock feedthrough
- Dynamic logic cascade solution

 Issues in Dynamic Design 2: Charge Sharing





Could we move it to there?

Charge stored originally on C_L is redistributed (shared) over C_L and C_A leading to reduced robustness

Charge Sharing

 
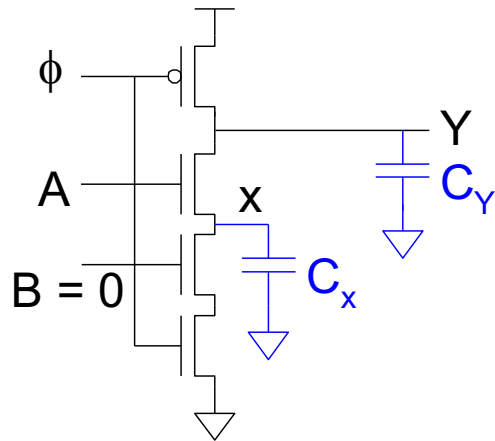
- Dynamic gates suffer from charge sharing



$$V_x = V_Y =$$


Charge Sharing

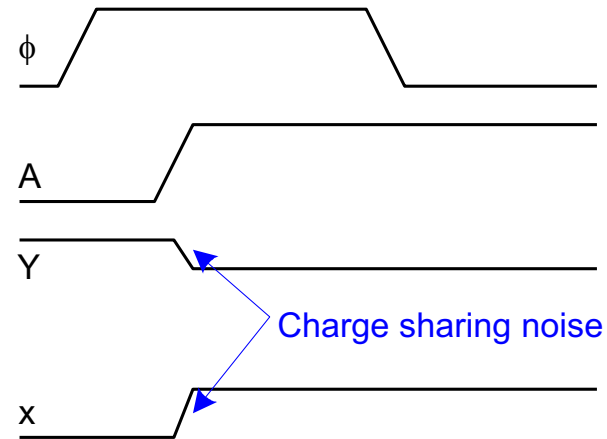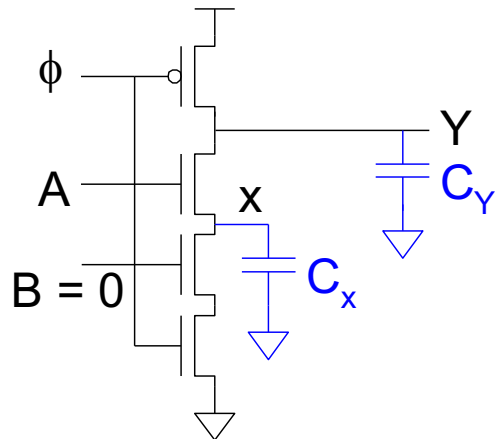- Dynamic gates suffer from charge sharing



$$V_x = V_Y = \frac{C_Y}{C_x + C_Y} V_{DD}$$

Solution to Charge Redistribution

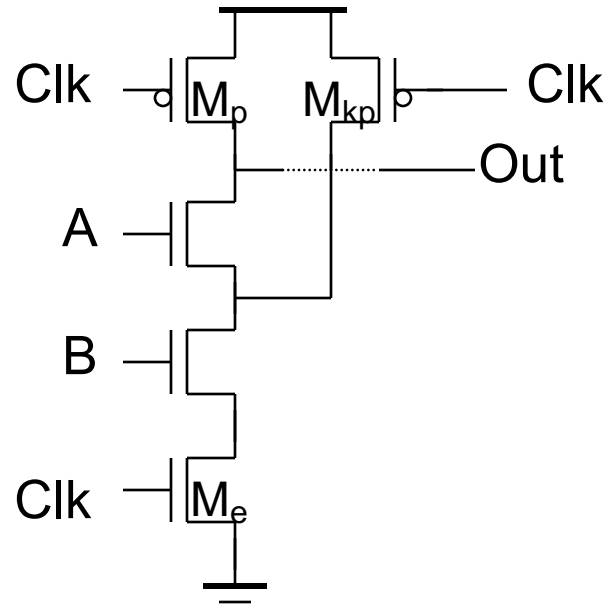


*Precharge internal nodes using a clock-driven transistor
(at the cost of increased area and power)*


Dynamic logic outline

- Dynamic logic principle
- Dynamic logic properties
- ***Dynamic logic design issues***
 - Charge-leakage
 - Charge-sharing
 - ***Backgate Coupling***
 - Clock feedthrough
- Dynamic logic cascade solution

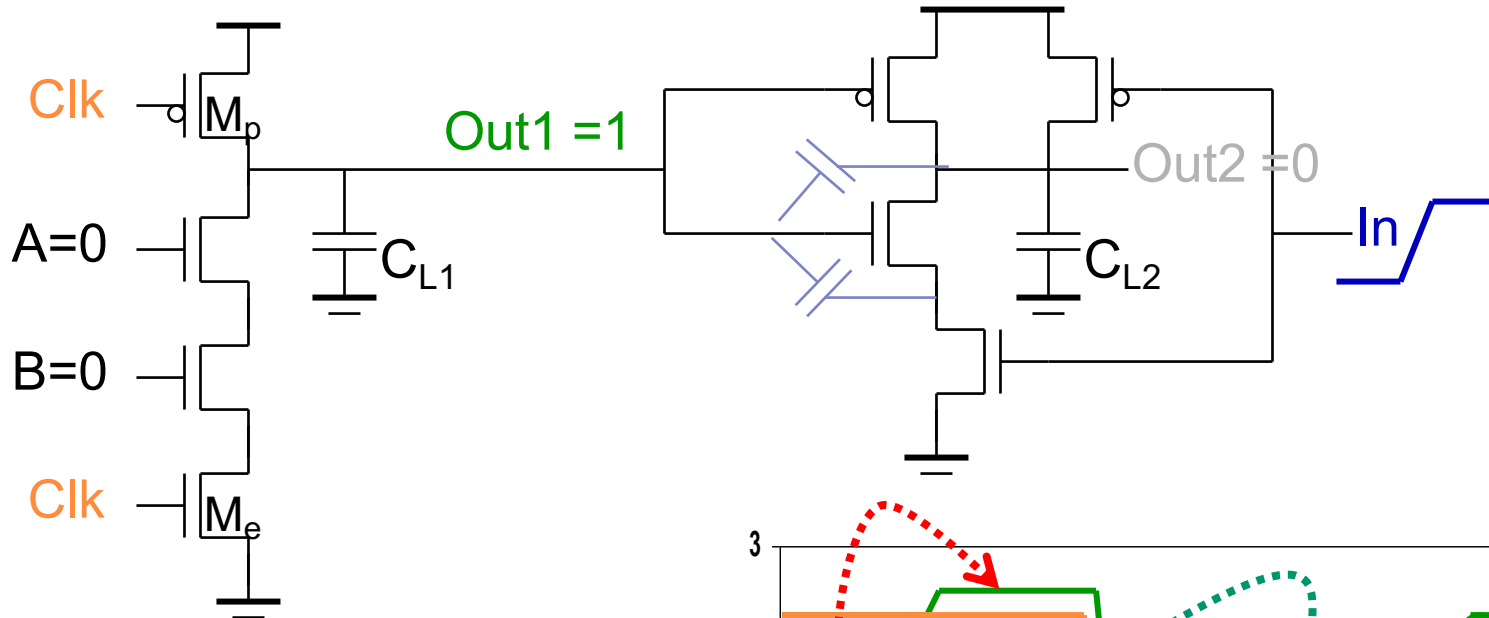Issues in Dynamic Design 3: Backgate Coupling




Dynamic NAND

 

Dynamic logic outline



- Dynamic logic principle
- Dynamic logic properties
- ***Dynamic logic design issues***
 - Charge-leakage
 - Charge-sharing
 - Backgate Coupling
 - ***Clock feedthrough***
- Dynamic logic cascade solution

 Issues in Dynamic Design 4: Clock Feedthrough




Coupling between **Out** and **Clk** input of the precharge device due to the gate to drain capacitance. So voltage of Out can rise above V_{DD} . The fast rising (and falling edges) of the clock **couple** to Out.

Clock Feedthrough

  

Crosstalk Noise Effects

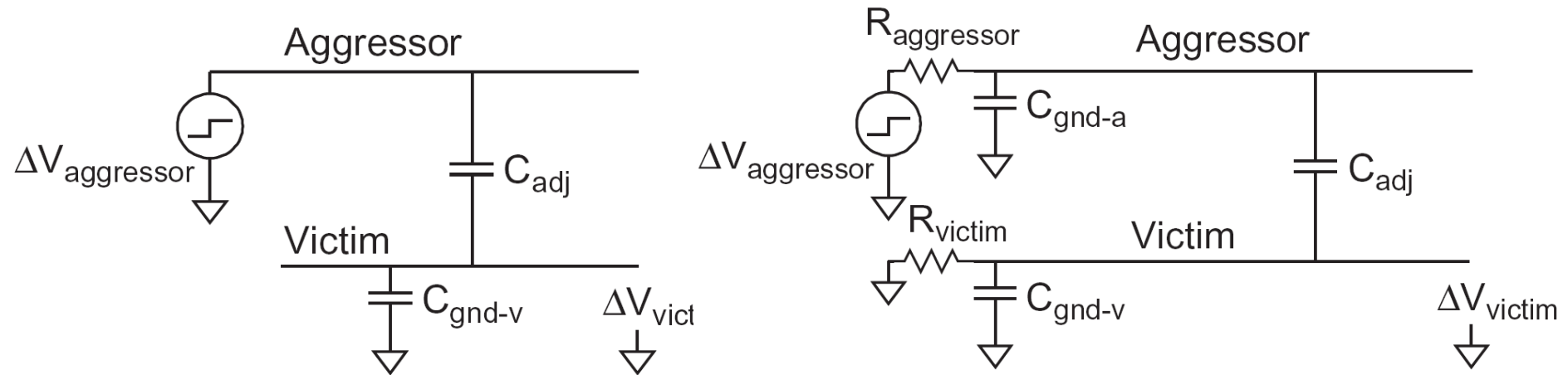


$$\Delta V_{victim} = \frac{C_{adj}}{C_{gnd-v} + C_{adj}} \Delta V_{aggressor}$$

$$k = \frac{\tau_{aggressor}}{\tau_{victim}} = \frac{R_{aggressor}(C_{gnd-a} + C_{adj})}{R_{victim}(C_{gnd-v} + C_{adj})}$$

$$\Delta V_{victim} = \frac{C_{adj}}{C_{gnd-v} + C_{adj}} \frac{1}{1 + k} \Delta V_{aggressor}$$

Waveforms of coupling noise

 


Dynamic logic outline

- Dynamic logic principle
- Dynamic logic properties
- Dynamic logic design issues
 - Charge-leakage
 - Charge-sharing
 - Backgate Coupling
 - Clock feedthrough
- **Dynamic logic cascade solution**

Dynamic logic outline

- Dynamic logic principle
- Dynamic logic properties
- Dynamic logic design issues
 - Charge-leakage
 - Charge-sharing
 - Backgate Coupling
 - Clock feedthrough
- ***Dynamic logic cascade solution***


Cascading Dynamic Gates

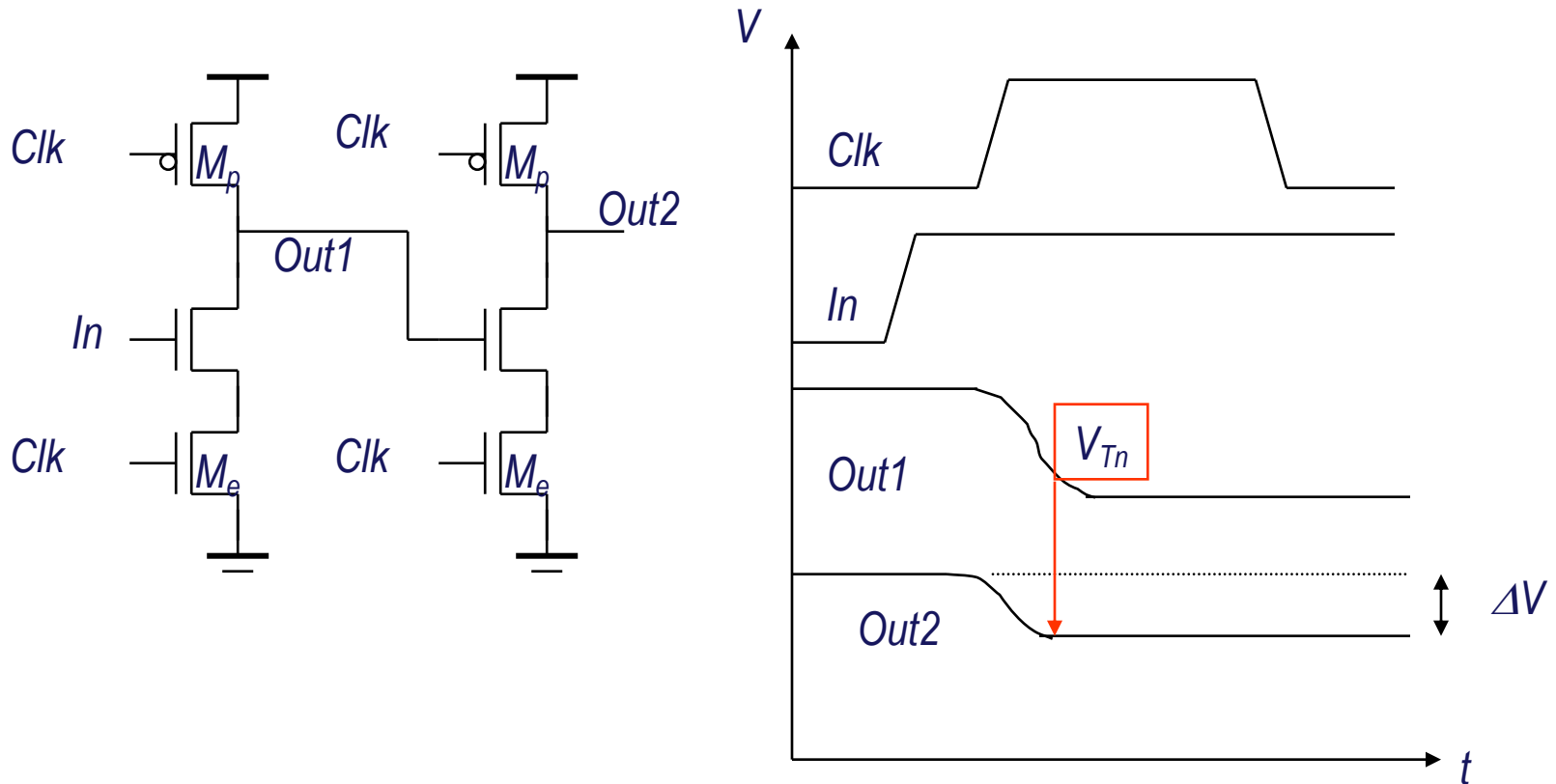

Only 0 → 1 transitions allowed at inputs!




Not 1 → 0!

Domino Logic

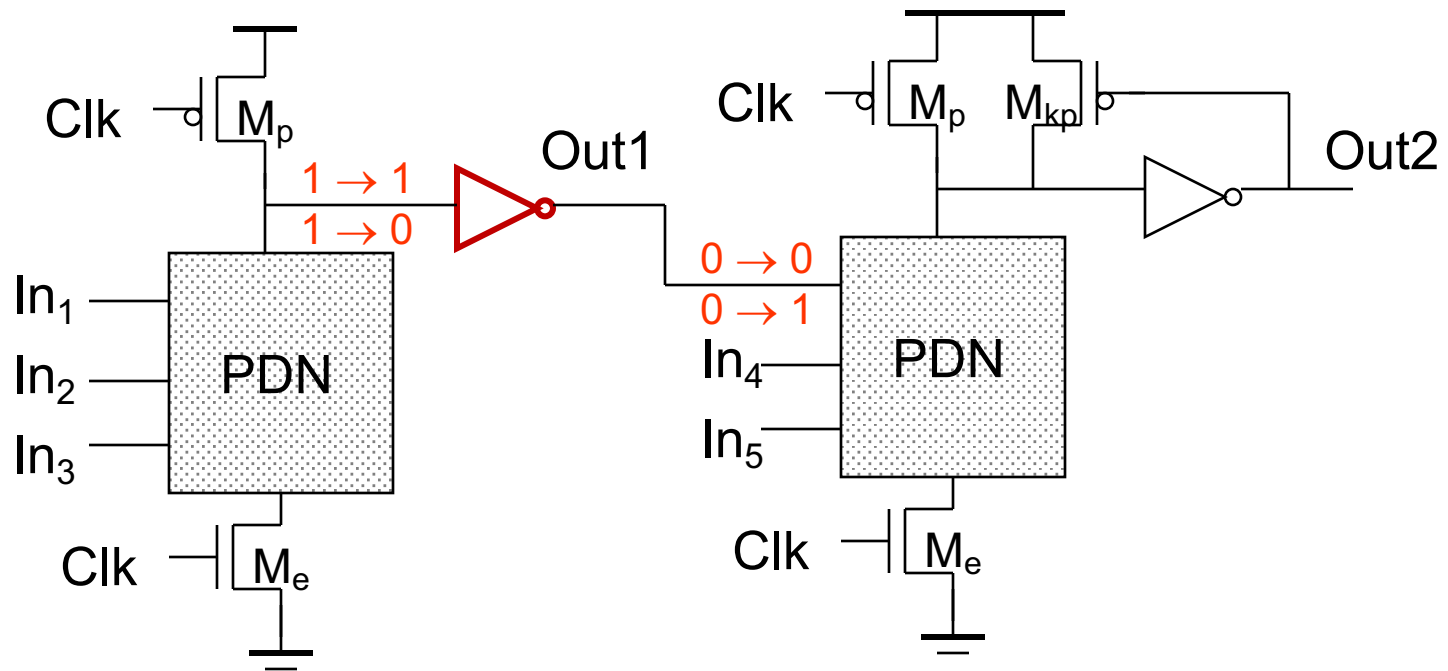


Domino Gates

 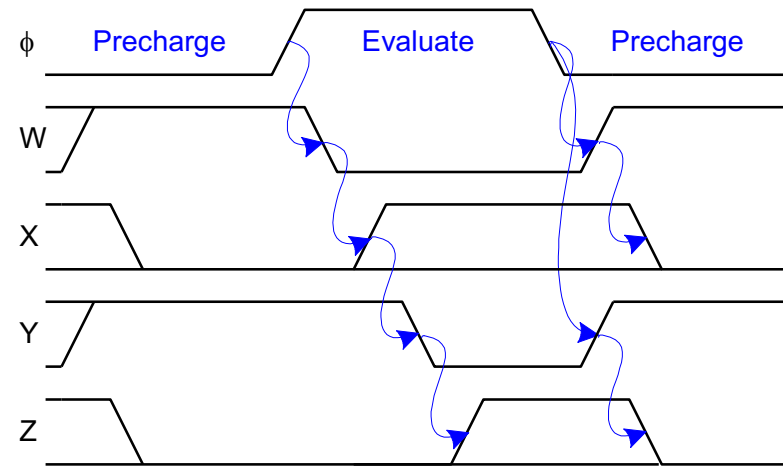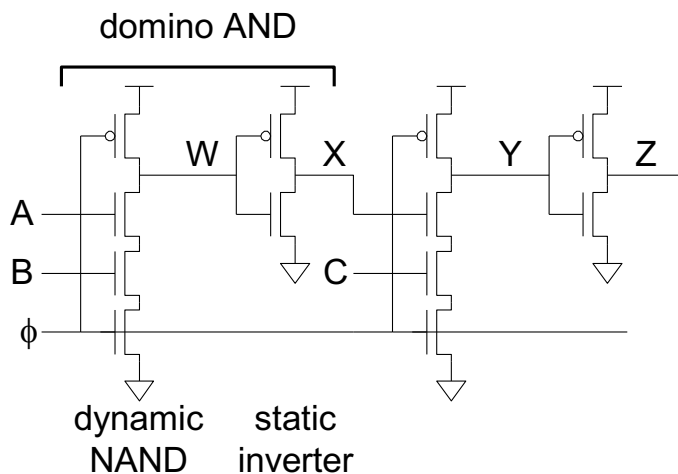- Follow dynamic stage with inverting static gate
 - Dynamic / static pair is called domino gate
 - Produces monotonic outputs




Why Domino?

 


Like falling dominos!

Designing with Domino Logic

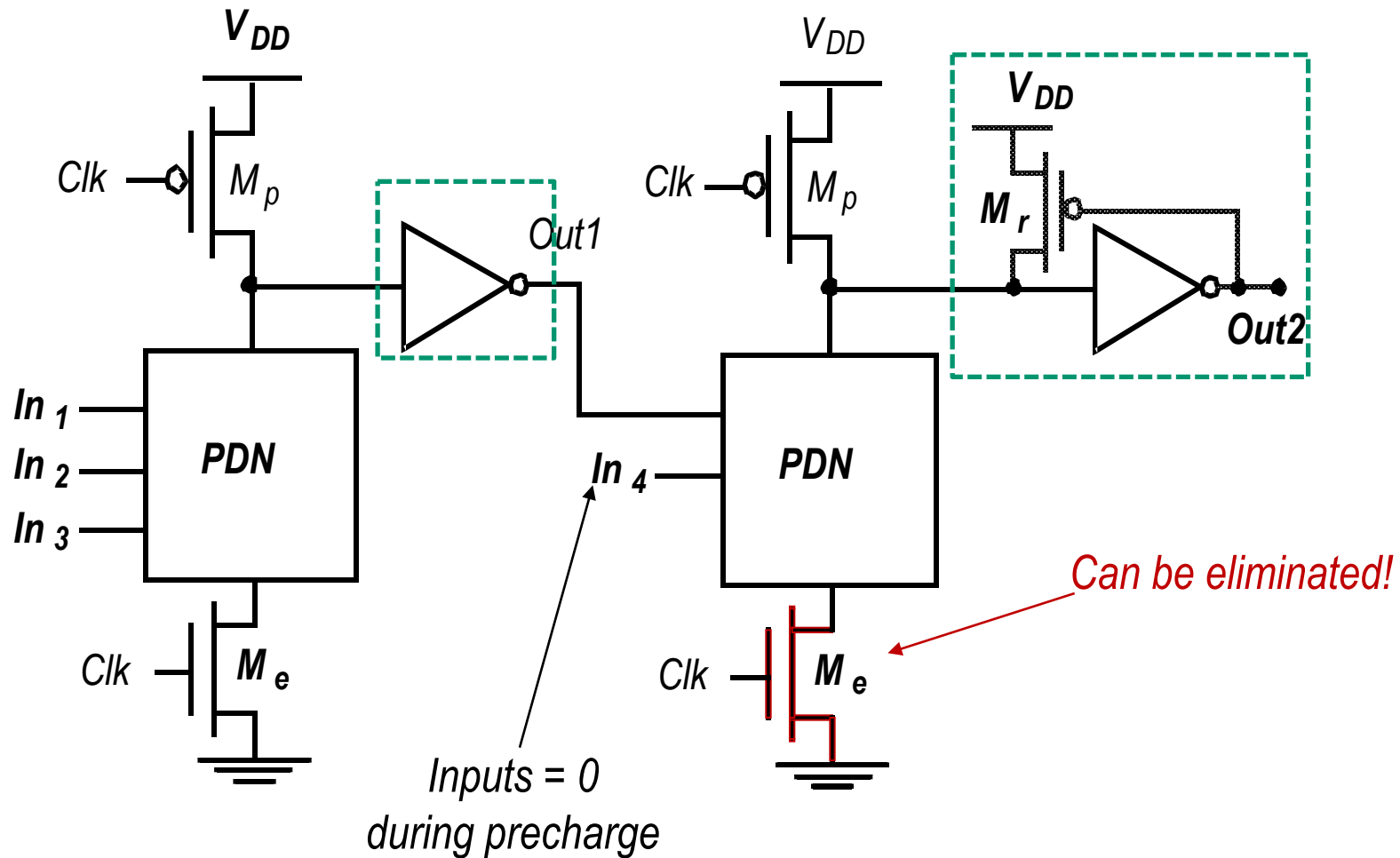


Footless Domino

 

- *The first gate in the chain needs a foot switch*
- ***Precharge is rippling – short-circuit current***
- *A solution is to delay the clock for each stage*

np-CMOS

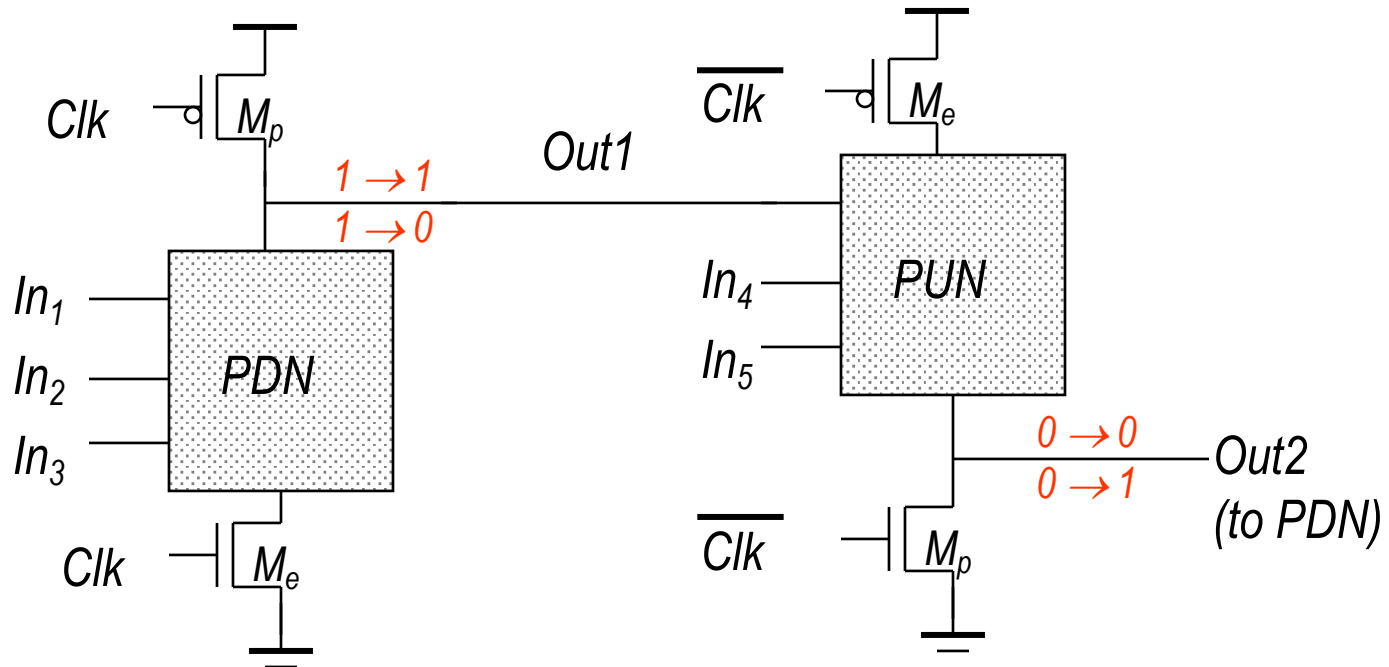

Only $0 \rightarrow 1$ transitions allowed at inputs of PDN
Only $1 \rightarrow 0$ transitions allowed at inputs of PUN

Domino Summary

- Domino logic is attractive for high-speed circuits
 - 1.5 – 2x faster than static CMOS
 - But many challenges:
 - Monotonicity
 - Leakage
 - Charge sharing
 - Noise
- Widely used in high-performance microprocessors

Traditional Domino Circuits

- Ping-pang approach for overlapping the precharge time

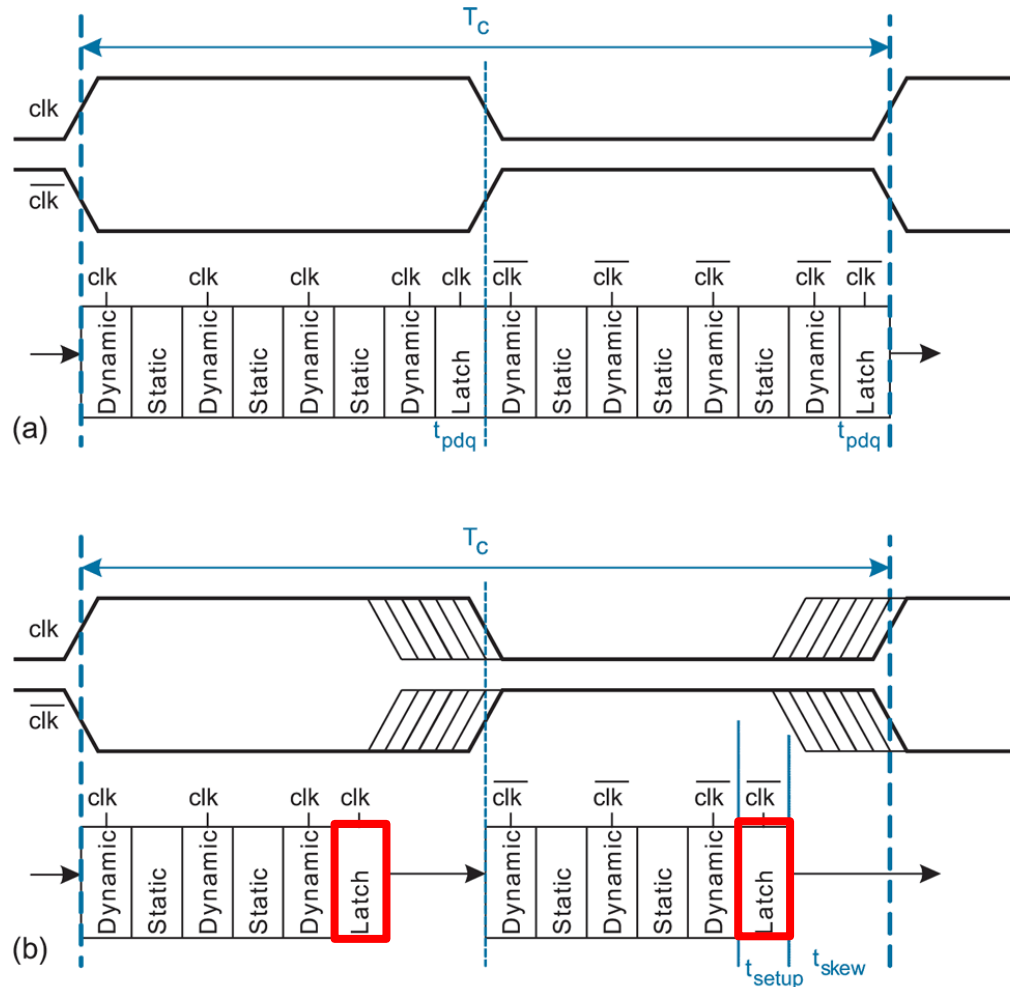


FIG 7.43 Traditional domino circuits

Some circuits pitfalls


Faults... ..



Outline

- Circuit Pitfalls
 - Detective puzzle
 - Given circuit and symptom, diagnose cause and recommend solution
 - All these pitfalls have caused failures in real chips


Bad Circuit 1

 

Symptom

Mux works $Y=1$ when selected =1 but D=1.

Bad Circuit 1

 


Symptom

Mux works $Y=1$ when selected =1 but $D=1$.

❑ Principle: Threshold drop

- X never rises above $V_{DD} - V_t$
- V_t is raised by the body effect $V_t = V_{t0} + \gamma(\sqrt{|-2\Phi_F + V_{SB}|} - \sqrt{|2\Phi_F|})$
- The threshold drop is most serious as V_t becomes a greater fraction of V_{DD} .

Bad Circuit 1

 


Symptom

Mux works Y=1 when selected =1 but D=1.

- Principle: Threshold drop $V_t = V_{t0} + \gamma(\sqrt{|-2\Phi_F + V_{SB}|} - \sqrt{|2\Phi_F|})$
 - X never rises above $V_{DD} - V_t$
 - V_t is raised by the body effect
 - The threshold drop is most serious as V_t becomes a greater fraction of V_{DD} .

Bad Circuit 1

 


Symptom

Mux works **Y=1** when selected =1 but D=1.

- Principle: Threshold drop $V_t = V_{t0} + \gamma(\sqrt{|-2\Phi_F + V_{SB}|} - \sqrt{|2\Phi_F|})$
 - X never rises above $V_{DD} - V_t$
 - V_t is raised by the body effect
 - The threshold drop is most serious as V_t becomes a greater fraction of V_{DD} .
- Solution: Use transmission gates, not pass transistors

Bad Circuit 2

 


Symptom

Precharge gate ($Y=0$)

Then evaluate

**Eventually Y
spontaneously flips to 1**

Bad Circuit 2

 

Symptom


Precharge gate ($Y=0$)

Then evaluate

**Eventually Y
spontaneously flips to 1**

- Principle: Leakage
 - X is a dynamic node holding value as charge on the node
 - Eventually subthreshold leakage may disturb charge
- Solution:

Bad Circuit 2

 


Symptom

Precharge gate ($Y=0$)


Then evaluate

**Eventually Y
spontaneously flips to 1**

 - Principle: Leakage
 - X is a dynamic node holding value as charge on the node
 - Eventually subthreshold leakage may disturb charge
- Solution:




Bad Circuit 3

 

Symptom

When only one input is true, **$Y = 0$** .

Bad Circuit 3

 


Symptom

When only one input is true, **$Y = 0$** .

- Principle: Ratio Failure
 - nMOS and pMOS fight each other.
 - If the pMOS is too strong, nMOS cannot pull X low enough.
- Solution:

Bad Circuit 3

 


Symptom

When only one input is true, **$Y = 0$** .

- Principle: Ratio Failure
 - nMOS and pMOS fight each other.
 - If the pMOS is too strong, nMOS cannot pull X low enough.
- Solution: Check that ratio is satisfied in all corners

Bad Circuit 4

 


Symptom

Precharge gate while
 $A = B = 0$, so $Z = 0$ Set $f = 1$

A rises

Z is observed to sometimes rise

Bad Circuit 4

 


Symptom

Precharge gate while
 $A = B = 0$, so $Z = 0$ Set $f = 1$


A rises

Z is observed to sometimes rise

 - Principle: Charge Sharing
 - If X was low, it shares charge with Y



Bad Circuit 4

 


Symptom

Precharge gate while
 $A = B = 0$, so $Z = 0$ Set $f = 1$

A rises

Z is observed to sometimes rise

 - Principle: Charge Sharing
 - If X was low, it shares charge with Y
- Solutions: Limit charge sharing
 - Safe if $C_Y \gg C_X$ $V_x = V_Y = \frac{C_Y}{C_x + C_Y} V_{DD}$
 - Or precharge node X too



Summary

- Static CMOS gates are very robust
 - Logic effect/Fan-in relate to the delay/Power evaluation
- Other circuits suffer from a variety of pitfalls
 - Pseudo NMOS logic
 - Pass transistor
 - cascade problem ,restorer(keeper),some pass logic
 - Dynamic logic
 - Characteristic
 - Cascade issue
 - Domino logic
 - Some pitfalls of dynamic logic