 


Chapter 3 Inverter Review



summary

- CMOS static behavior
 - VTC, noise margin, threshold voltage
- CMOS dynamic behavior
 - Capacitance mosaic, delay
 - Ratio pMOS/nMOS:3.5,2.4,1.6
 - Optimizing inverter sizing
- Power
 - Power mosaic
 - Optimizing dynamic power
 - Short power consideration

CMOS Inverter Load Characteristics



CMOS Inverter VTC

  

Summary of CMOS inverter operation

Region	Condition	P-device	N-device	output
A	$[0, V_{tn}]$	linear	cutoff	V_{DD}
B	$[V_{tn}, V_{DD}/2]$	linear	saturated	$V_{DD}/2$
C	$= V_{DD}/2$	saturated	saturated	X drop
D	$[V_{DD}/2, V_{DD} - V_{TP}]$	saturated	linear	$< V_{DD}/2$
E	$[V_{DD} - V_{TP} , V_{DD}]$	cutoff	linear	0

CMOS properties

- High noise margins, the voltage swing is equal to the supply voltage
- Ratioless circuit structure
- Low output impedance
- High input resistance
- Low power

CMOS inverter static behavior

- *Threshold Voltage*
- Noise Margin
- Gain
- DC robust

$$I_{ds} = \mu_n C_{ox} \frac{W}{L} \left((V_{gs} - V_T) V_{dsat} - \frac{V_{dsat}^2}{2} \right) \quad k_n = \beta_n = \mu_n C_{ox} \frac{W}{L}$$


$$k_n \left((V_{gsn} - V_{Tn}) V_{dsatn} - \frac{V_{dsatn}^2}{2} \right) + k_p \left((V_{gsp} - V_{Tp}) V_{dsatp} - \frac{V_{dsatp}^2}{2} \right) = 0$$

$$k_n \left((V_M - V_{Tn}) V_{dsatn} - \frac{V_{dsatn}^2}{2} \right) + k_p \left((V_M - V_D - V_{Tp}) V_{dsatp} - \frac{V_{dsatp}^2}{2} \right) = 0$$

$$V_M = \frac{\left(V_{Tn} + \frac{V_{dsatn}}{2} \right) + \gamma \left(V_{DD} + V_{Tp} + \frac{V_{dsatp}}{2} \right)}{1 + \gamma} \approx \frac{\gamma V_{DD}}{1 + \gamma}$$


$$\gamma = \frac{k_p V_{dsatp}}{k_n V_{dsatn}} = \frac{W_p v_{dsatp}}{W_n v_{dsatn}}$$
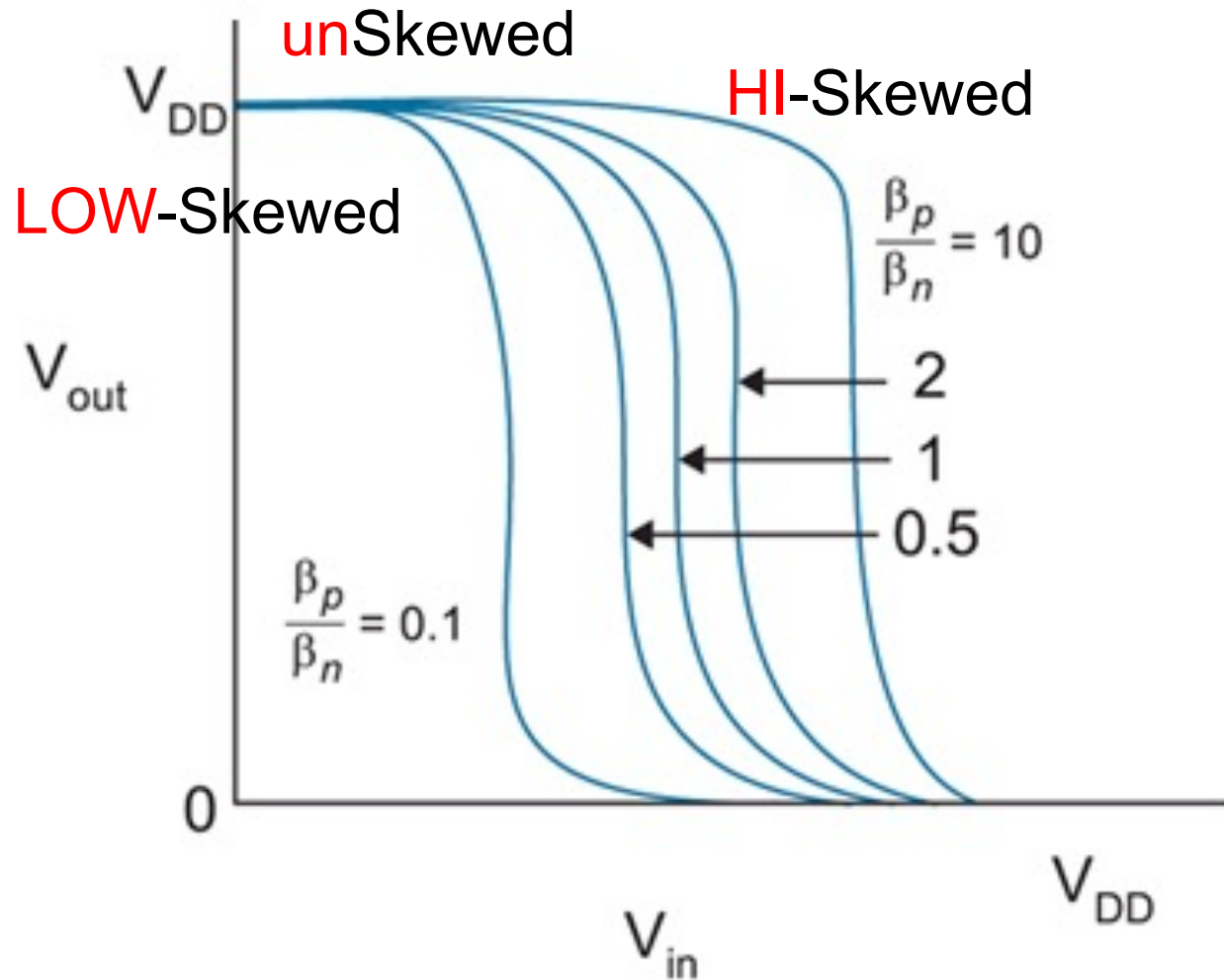
$$V_{sat} \approx V_c = L E_c = L \frac{2 v_{sat}}{\mu_{eff}}$$



$$V_M = \frac{\left(V_{Tn} + \frac{V_{dsatn}}{2}\right) + \gamma(V_{DD} + V_{Tp} + \frac{V_{dsatp}}{2})}{1 + \gamma} \approx \frac{\gamma V_{DD}}{1 + \gamma}$$

 Switching Threshold as a function of Transistor Ratio



$$I_{ds} = \mu_n C_{ox} \frac{W}{L} \left((V_{gs} - V_T) V_{dsat} - \frac{V_{dsat}^2}{2} \right) \quad k_n = \beta_n = \mu_n C_{ox} \frac{W}{L}$$

$$k_n \left((V_{gsn} - V_{Tn}) V_{dsat_n} - \frac{V_{dsat_n}^2}{2} \right) + k_p \left((V_{gsp} - V_{Tp}) V_{dsat_p} - \frac{V_{dsat_p}^2}{2} \right) = 0$$

$$k_n \left((V_M - V_{Tn}) V_{dsat_n} - \frac{V_{dsat_n}^2}{2} \right) + k_p \left((V_M - V_D - V_{Tp}) V_{dsat_p} - \frac{V_{dsat_p}^2}{2} \right) =$$

$$\frac{W_p/L_p}{W_n/L_n} \approx \frac{k'_n V_{dsat_n} \left(V_M - V_{Tn} - \frac{V_{dsat_n}}{2} \right)}{k'_p V_{dsat_p} \left(V_{DD} - V_M + V_{Tp} + \frac{V_{dsat_p}}{2} \right)}$$

Switching threshold of CMOS inverter

Parameters for manual model of generic 0.25um CMOS process(minimum length device)

	$V_{T0}(V)$	$\gamma(V^{0.5})$	$V_{DSAT}(V)$	$k'(A/V^2)$	$\lambda(V^{-1})$
<i>NMOS</i>	0.43	0.4	0.63	115×10^{-6}	0.06
<i>PMOS</i>	-0.4	-0.4	-1	-30×10^{-6}	-0.1

Assuming $W_p/W_n=8$, calculating $V_M=?$

$$r = \frac{k'_p \frac{W_p}{L_p} V_{DSAT_p}}{k'_n \frac{W_n}{L_n} V_{DSAT_n}} = \frac{-30 * (-1)}{115 * 0.63} * 8 = 3.3$$

$$V_M = \frac{(V_{Tn} + \frac{V_{DSAT_n}}{2}) + r(V_{DD} + V_{Tp} + \frac{V_{DSAT_p}}{2})}{1 + r}$$

$$= \frac{(0.43 + \frac{0.63}{2}) + 3.3(2.5 - 0.4 - \frac{0.4}{2})}{1 + 3.3} = \frac{0.75 + 3.3 * 1.9}{1 + 3.3} = 1.63V$$

Switching threshold of CMOS inverter

Parameters for manual model of generic 0.25um CMOS process(minimum length device)

	$V_{T0}(V)$	$\gamma(V^{0.5})$	$V_{DSAT}(V)$	$k'(A/V^2)$	$\lambda(V^{-1})$
<i>NMOS</i>	0.43	0.4	0.63	115×10^{-6}	0.06
<i>PMOS</i>	-0.4	-0.4	-1	-30×10^{-6}	-0.1


$$\frac{(W/L)_p}{(W/L)_n} = \frac{k'_n V_{DSAT_n} (V_M - V_{Tn} - \frac{V_{DSAT_n}}{2})}{-k'_p V_{DSAT_p} (V_{DD} - V_M + V_{Tp} + \frac{V_{DSAT_p}}{2})} = \frac{115 \times 10^{-6} \times 0.63 \times (1.25 - 0.43 - \frac{0.63}{2})}{30 \times 10^{-6} \times 1 \times (1.25 - 0.4 - \frac{1}{2})} = 3.5$$

This rate let $V_M = V_{dd}/2$!

CMOS inverter static behavior


- Threshold Voltage
- ***Noise Margin***
- Gain
- DC robust

Determining V_{IH} and V_{IL}

 

Determining V_{IH} and V_{IL}

A simplified approach!

 

$$V_{IH} - V_{IL} = -\frac{(V_{OH} - V_{OL})}{g} = \frac{-V_{DD}}{g}$$

$$V_{IH} = V_M - \frac{V_M}{g}, V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

$$NM_H = V_{DD} - V_{IH}, NM_L = V_{IL}$$

V_M increase, NM_H decrease, NM_L increase

Example

$g=-30$, $V_{dd}=2.5V$, $V_M=1.0V$ Please estimate NM_H and NM_L

$$V_{IH} = V_M - V_M/g = 1.0 * (1 + 1/30) = 1.03V$$

$$V_{IL} = (V_{DD} - V_M)/g + V_M = -1.5/30 + 1.0 = 0.95V$$


$$NM_H = V_{OH} - V_{IH} = 2.5 - 1.03 = 1.47V$$

$$NM_L = V_{IL} - V_{OL} = 0.95V$$


CMOS inverter static behavior

- Threshold Voltage
- Noise Margin
- *Gain*
- DC robust

Inverter Gain

 
 
$$k_n V_{DSAT_n} (V_{in} - V_{Tn} - \frac{V_{DSAT_n}}{2})(1 + \lambda V_{out}) + k_p V_{DSAT_p} (V_{in} - V_{DD} - V_{Tp} - \frac{V_{DSAT_p}}{2})(1 + \lambda(V_{DD} - V_{out})) = 0$$




Inverter Gain

$$\begin{aligned}
 g &= \left. \frac{dV_{out}}{dV_{in}} \right|_{V_{in}=V_M} \\
 &= - \left. \frac{k_n V_{DSATn} (1 + \lambda_n V_{out}) + k_p V_{DSATp} (1 + \lambda_p V_{out} - \lambda_p V_{DD})}{\lambda_n k_n V_{DSATn} \left(V_{in} - V_{Tn} - V_{DSATn}/2 \right) + \lambda_p k_p V_{DSATp} \left(V_{in} - V_{DD} - V_{Tp} - V_{DSATp}/2 \right)} \right|_{V_{in}=V_M} \\
 &\approx - \frac{k_n V_{DSATn} (1 + \lambda_n V_{out}) + k_p V_{DSATp} (1 + \lambda_p V_{out} - \lambda_p V_{DD})}{k_n V_{DSATn} \left(V_{in} - V_{Tn} - V_{DSATn}/2 \right) (\lambda_n - \lambda_p)} \\
 &= - \frac{1 + \gamma}{\left(V_M - V_{Tn} - V_{DSATn}/2 \right) (\lambda_n - \lambda_p)}
 \end{aligned}$$

Ratio increase, Gain increase

$$\gamma = \frac{k'_p \frac{W_p}{L_p} V_{DSATp}}{k'_n \frac{W_n}{L_n} V_{DSATn}}$$

 

homework1

An inverter in the generic 0.25um CMOS technology designed with a PMOS-to-NMOS ratio of **64** and with the NMOS transistor minimum size ($W=0.375\mu\text{m}$, $L=0.25\mu\text{m}$, $W/L=1.5$), $V_{DD}=2.5\text{V}$, Please give the gain of V_M , and V_{IL} , V_{IH} , NM_L , NM_H , **VTC** curve

Parameters for manual model of generic 0.25um CMOS process(minimum length device)

	$V_{T0}(V)$	$\gamma(V^{0.5})$	$V_{DSAT}(V)$	$k'(A/V^2)$	$\lambda(V^{-1})$
<i>NMOS</i>	0.43	0.4	0.63	115×10^{-6}	0.06
<i>PMOS</i>	-0.4	-0.4	-1	-30×10^{-6}	-0.1

$$V_M = \frac{\left(V_{Tn} + V_{DSATn}/2\right) + \gamma(V_{DD} + V_{Tp} + V_{DSATp}/2)}{1 + \gamma}$$

$$= \frac{(0.43 + 0.63/2) + 26.4 * (2.5 - 0.4 - 1/2)}{1 + 26.4}$$

$$= \frac{0.745 + 26.4 * 1.6}{1 + 26.4} = 1.57$$

$$g = - \frac{1 + \gamma}{\left(V_M - V_{Tn} - V_{DSATn}/2\right) (\lambda_n + \lambda_p)} = - \frac{1 + 26.4}{\left(1.57 - 0.43 - \frac{0.63}{2}\right) (0.06 + 0.1)}$$

$$= - \frac{27.4}{0.824 * 0.16} = -208$$

$$\gamma = \frac{k'_p W_p / L_p V_{DSATp}}{k'_n W_n / L_n V_{DSATn}} = \frac{-30 * (-1)}{115 * 0.63} * 64 = 26.4$$

$$V_{IH} = V_M - V_M / g = 1.57 * (1 + 1/208) = 1.58V$$

$$V_{IL} = (V_{DD} - V_M) / g + V_M = -0.93 / 208 + 1.57 = 1.57V$$





$$NM_H = V_{OH} - V_{IH} = 2.5 - 1.58 = 0.92V$$

$$NM_L = V_{IL} - V_{OL} = 1.57V$$

C_{inverter} dynamic characteristic

- ***Capacitances mosaic***
- Propagation delay
- Optimizing inverter sizing

Computing the Capacitances

    

Capacitance model


$$C_{GS} = C_{GSO} + C_{GCS}$$

$$C_{GD} = C_{GDO} + C_{GCD}$$


$$C_{GB} = C_{GCB}$$

$$C_{SB} = C_{Sdiff}$$

$$C_{DB} = C_{Ddiff}$$

 


The Miller Effect

 


“A capacitor experiencing identical but opposite voltage swings at both its terminals can be replaced by a capacitor to ground, whose value is two times the original value.”

Computing the Capacitances

 
 
$$AD = 4*4 + 3*1 = 16 + 3 = 19\lambda^2$$
$$PD = 1 + 4 + 4 + 4 + 1 + 1 = 15\lambda$$



Computing the Capacitances

capacitor	expression	Value(fF) (H->L)	Value(fF) (L->H)
C_{gd1}	$2C_{GDO_n} * W_n$	0.23	0.23
C_{gd2}	$2C_{GDO_p} * W_p$	0.61	0.61
C_{db1}	$K_{eqn}AD_nC_J + K_{eqwn}PD_nC_{JSW}$	0.66	0.90
C_{db2}	$K_{eqn}AD_nC_J + K_{eqwn}PD_nC_{JSW}$	1.5	1.15
C_{g3}	$(C_{GDO_n} + C_{GSO_n})W_n + C_{ox}W_nL_n$	0.76	0.76
C_{g4}	$(C_{GDO_p} + C_{GSO_p})W_p + C_{ox}W_pL_p$	2.28	2.28
C_w		0.12	0.12
C_L		6.1	6.0

$$C_j = \frac{dQ_j}{dV_D} = \frac{C_{j_0}}{(1 - V_D/\Phi_0)^m}$$

$$C_L = W_n C_n + W_p C_p + C_w$$

Cinverter dynamic characteristic

- Capacitances mosaic
- ***Propagation delay***
- Optimizing inverter sizing

Define NMOS-to-PMOS ratio

$$C_L = W_n C_n + W_p C_p + C_w$$

$$t_{pHL} = \ln 2 C_L R_{eqn} \approx \frac{C_L}{2 \left(\frac{W}{L} \right)_n k'_n V_{dsatn}} \approx \frac{C_n}{2 k'_n V_{dsatn}} + \frac{\beta C_p}{2 k'_n V_{dsatn}}$$

$$t_{pLH} = \ln 2 C_L R_{eqp} \approx \frac{C_L}{2 \left(\frac{W}{L} \right)_p k'_p V_{dsatp}} \approx \frac{C_p}{2 k'_p V_{dsatp}} + \frac{C_n}{2 \beta k'_p V_{dsatp}}$$

In order to create an inverter with a symmetrical propagate delays $\gamma = \frac{R_{eqp}}{R_{eqn}} = \frac{\left(\frac{W}{L} \right)_n k'_n V_{DSATn}}{\left(\frac{W}{L} \right)_p k'_p V_{DSATp}} = 1$


Also create symmetrical VTC

$\beta = 2.4$ which $R_n = R_p$!

Parameters for manual model of generic 0.25um CMOS process(minimum length device)

	$V_{To}(V)$	$\gamma(V^{0.5})$	$V_{DSAT}(V)$	$k'(A/V^2)$	$\lambda(V^{-1})$
NMOS	0.43	0.4	0.63	115×10^{-6}	0.06
PMOS	-0.4	-0.4	-1	-30×10^{-6}	-0.1

Which point is optimal delay?

 

Design for Performance

- Reduce C_L
 - internal diffusion capacitance of the gate itself , keep the drain diffusion as small as possible
 - interconnect capacitance
 - fanout
- Increase V_{DD}
 - can trade-off energy for performance
 - *increasing V_{DD} above a certain level yields only very minimal improvements*
- Increase W/L ratio of the transistor
 - the most powerful and effective performance optimization tool in the hands of the designer
 - watch out for **self-loading!** – when the intrinsic capacitance dominates the extrinsic load


Which point is optimal delay?

$$C_L = (C_{d_{n1}} + C_{d_{p1}}) + 2(C_{g_{n3}} + C_{g_{p4}}) + C_w = (1 + \beta)(C_{d_{n1}} + 2C_{g_{n3}}) + C_w$$

$$= (1 + \beta)C_s + C_w$$

$$C_s = C_{d_{n1}} + 2C_{g_{n3}}$$

$$\beta = \frac{(W/L)_p}{(W/L)_n}$$

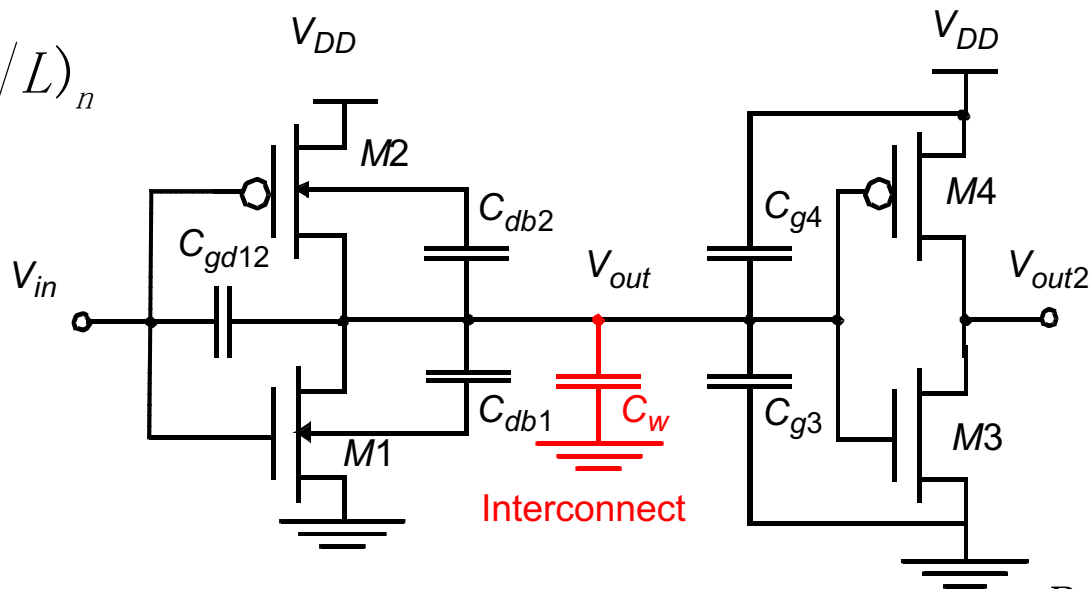

$$t_p = \frac{t_{pLH} + t_{pHL}}{2} = \frac{\ln 2}{2} ((1 + \beta)C_s + C_w) (R_{eq_n} + \frac{R_{eq_p}}{\beta})$$

$$= 0.345((1 + \beta)C_s + C_w)R_{eq_n}(1 + \frac{\gamma}{\beta})$$

Which point is optimal delay?

Table 3.3 Equivalent resistance R_{eq} ($W/L = 1$) of NMOS and PMOS transistors in 0.25 μm CMOS process (with $L = L_{min}$). For larger devices, divide R_{eq} by W/L .

V_{DD} (V)	1	1.5	2	2.5
NMOS (k Ω)	35	19	15	13
PMOS (k Ω)	115	55	38	31

$$\frac{\partial t_p}{\partial \beta} = 0$$

$$\frac{\partial [0.345((1 + \beta)C_s + C_w)R_{eq_n}(1 + \frac{\gamma}{\beta})]}{\partial \beta} = 0$$

$$\beta = \sqrt{\gamma(1 + \frac{C_w}{C_s})} \approx \sqrt{\gamma} = \sqrt{\frac{31}{13}} \Big|_{\substack{V_{dd}=2.5V \\ 0.25\mu m}} = 1.5$$

This r is different from before! It is the resistor rate of the NMOS and PMOS



Summary of Ratio

Beta=1.5, we have minimum delay

$$\beta = \sqrt{\gamma} \approx \sqrt{\frac{k'_n V_{DSat_n}}{k'_p V_{DSat_p}}}$$

Beta=2.4, we have equal delay $t_{phl}=t_{plh}$

$$\beta = \gamma = \frac{k'_n V_{DSat_n}}{k'_p V_{DSat_p}}$$

Beta=3.5, we have $V_M=V_{dd}/2$

$$\frac{(W/L)_p}{(W/L)_n} = \frac{k'_n V_{DSAT_n} (V_M - V_{Tn} - \frac{V_{DSAT_n}}{2})}{-k'_p V_{DSAT_p} (V_{DD} - V_M + V_{Tp} + \frac{V_{DSAT_p}}{2})} = \frac{115 \times 10^{-6} \times 0.63 \times (1.25 - 0.43 - \frac{0.63}{2})}{30 \times 10^{-6} \times 1 \times (1.25 - 0.4 - \frac{1}{2})} = 3.5$$

Cinverter dynamic characteristic

- Capacitances mosaic
- Propagation delay
- *Optimizing inverter sizing*

Increasing inverter performance by sizing the NMOS and PMOS

$$\begin{aligned} t_p &= 0.69 R_{eq} (C_{int} + C_{ext}) = 0.69 R_{eq} C_{int} (1 + C_{ext} / C_{int}) \\ &= 0.69 (R_{ref} / S) (S C_{iref}) (1 + C_{ext} / S C_{iref}) \\ &= t_{p0} + t_{p0} \frac{C_{ext}}{S C_{iref}} \end{aligned}$$

$= t_{p0} (1 + \frac{C_2}{C_1})$


If load

If no load


$S \gg 0$ will eliminate the impact of any external load

Intrinsic delay is independent of the sizing of the gate

Device Sizing

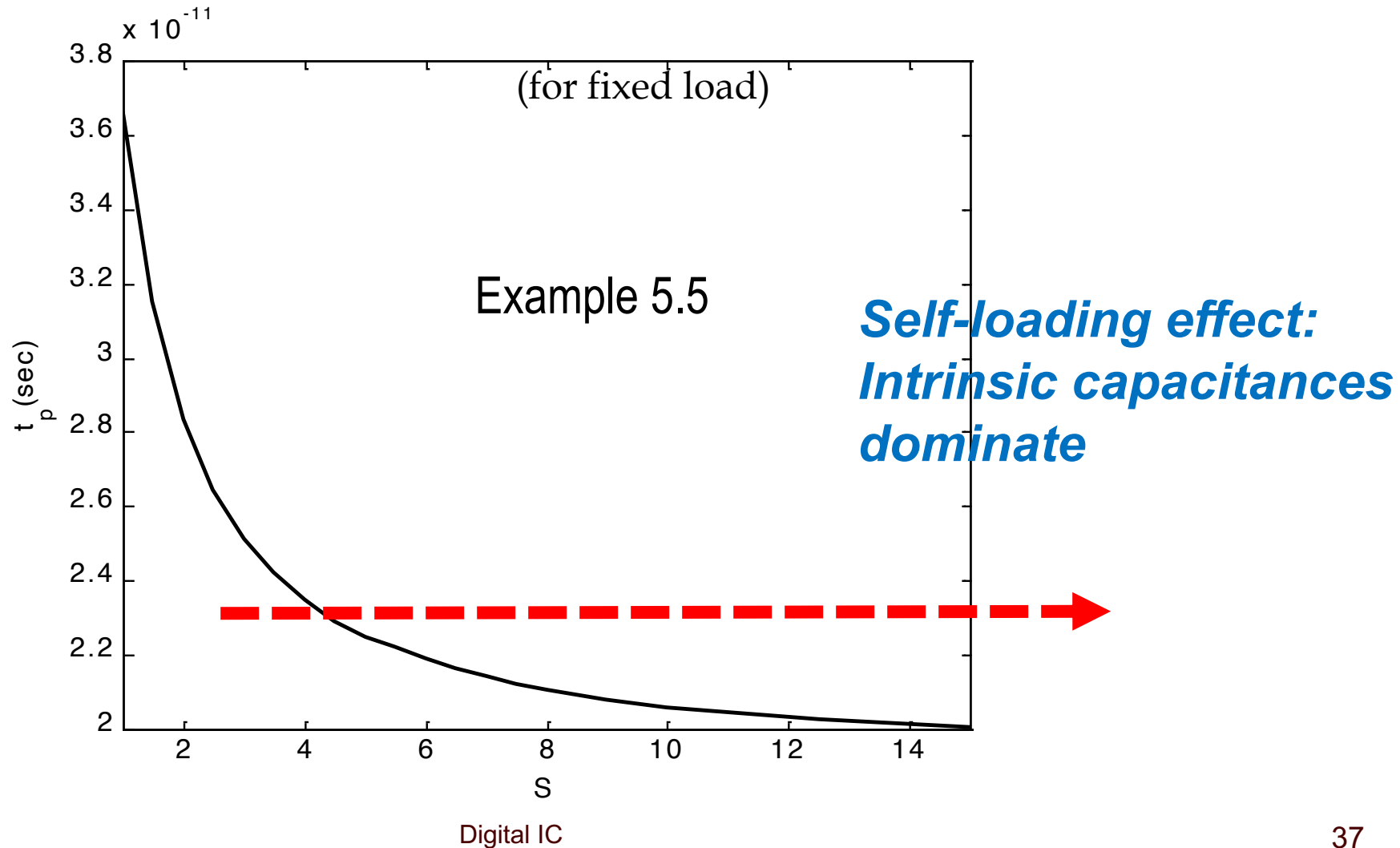

Apply to Inverter Chain

 

$$t_{pj} \sim R_{unit} C_{unit} \left(1 + \frac{C_{gin,j+1}}{\gamma C_{gin,j}} \right)$$

$$t_p = \sum_{j=1}^N t_{p,j} = t_{p0} \sum_{i=1}^N \left(1 + \frac{C_{gin,j+1}}{\gamma C_{gin,j}} \right), \quad C_{gin,N+1} = C_L$$

Optimal Tapering for Given N

- Delay equation has $N - 1$ unknowns, $C_{gin,2} - C_{gin,N}$
- Minimize the delay, find $N - 1$ partial derivatives

Result:
$$C_{gin,j+1}/C_{gin,j} = C_{gin,j}/C_{gin,j-1}$$

- Size of each stage is the geometric mean of two

neighbors
$$C_{gin,j} = \sqrt{C_{gin,j-1} C_{gin,j+1}}$$

- each stage has the same effective fanout (C_{out}/C_{in})
- ***each stage has the same delay***

Optimum size for fixed Number of Stages

When each stage is sized by f and has same eff. fanout f : $f^N = F = C_L / C_{gin,1}$

Effective fanout of each stage:

$$f = \sqrt[N]{F}$$

Minimum path delay

$$t_p = Nt_{p0} \left(1 + \sqrt[N]{F} / \gamma \right)$$

Where Does Power Go in CMOS?

- Dynamic Power Consumption
 - Charging and Discharging Capacitors
- Short Circuit Currents
 - Short Circuit Path between Supply Rails during Switching
- Leakage
 - Leaking diodes and transistors


Dynamic Power Consumption

- (dis)charge process
 - C_L is charged through pMOS on-resistance
 - C_L is discharged through nMOS on-resistance
- Power distribution
 - Charge processing: One part of Supply power is dissipated in the pMOS transistor, another part is dissipated in the charge C_L
 - Discharge processing: all dissipated in the nMOS transistor

Precise measure of dynamic power consumption

$$E_{V_{dd}} = \int_0^{\infty} i_{V_{dd}}(t) V_{dd} dt = V_{dd} \int_0^{\infty} C_L \frac{dv_{out}}{dt} dt$$
 
$$= C_L V_{dd} \int_0^{V_{dd}} dv_{out} = C_L V_{dd}^2$$



$$E_C = \int_0^{\infty} i_{V_{dd}}(t) v_{out} dt = \int_0^{\infty} C_L \frac{dv_{out}}{dt} v_{out} dt$$

$$= C_L \int_0^{V_{dd}} v_{out} dv_{out} = \frac{C_L V_{dd}^2}{2}$$

CMOS Energy & Power Equations

$$E = C_L V_{DD}^2 P_{0 \rightarrow 1} + t_{sc} V_{DD} I_{peak} + V_{DD} I_{leakage} 1/f_{clock}$$

$$f_{0 \rightarrow 1} = P_{0 \rightarrow 1} * f_{clock}$$

$$P = C_L V_{DD}^2 f_{0 \rightarrow 1} + t_{sc} V_{DD} I_{peak} f + V_{DD} I_{leakage}$$

Dynamic power

*Short-circuit
power*

Leakage power

Lowering Dynamic Power

Capacitance:
Function of fan-out, wire length, transistor sizes



Supply Voltage:
Has been dropping with successive generations

$$P_{\text{dyn}} = C_L V_{\text{DD}}^2 P_{0 \rightarrow 1} f$$

Activity factor:
How often, on average, do wires switch?

Clock frequency:
Increasing...

Short Circuit Power Consumption

  

Finite slope of the input signal causes a direct current path between V_{DD} and GND for a short period of time during switching when both the NMOS and PMOS transistors are conducting.


Short Circuit power consumption

- Energy of ever switch activity

$$E_{dp} = V_{dd} \frac{I_{peak}}{2} t_{rise} + V_{dd} \frac{I_{peak}}{2} t_{fall}$$

- Average power
 
$$P_{dp} = \frac{t_{rise} + t_{fall}}{2} V_{dd} I_{peak} f$$




- Short circuit occupy no more than 20% of dynamic power**


$$t_{sc} = \frac{V_{DD} - 2V_T}{V_{DD}} t_s \approx \frac{V_{DD} - 2V_T}{V_{DD}} \times \frac{t_{r(f)}}{0.8}$$

An example

 - Assume rise/fall time both are 300ps
- Short circuit power:
 $300\text{ps} \times 5\text{V} \times 0.14\text{mA} = 0.21\text{pJ}$
- Dynamic power
 $30\text{pF} \times 5\text{V} \times 5\text{V} = 0.75\text{pJ}$



Impact of C_L on P_{sc}

 


Large capacitive load

Output fall time significantly larger than input rise time.

Small capacitive load

Output fall time substantially smaller than the input rise time.

I_{peak} as a Function of C_L

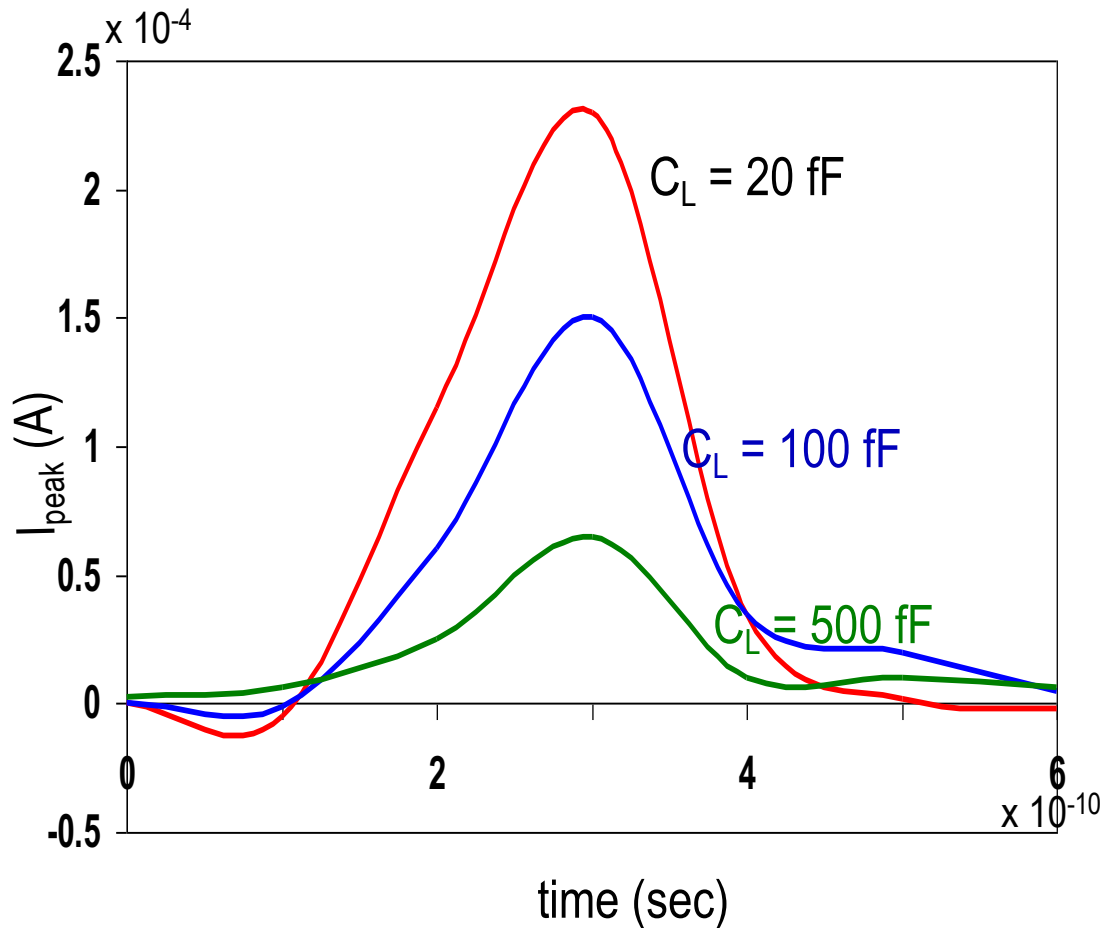


When load capacitance is small, I_{peak} is large.

Short circuit dissipation is minimized by matching the rise/fall times of the input and output signals - slope engineering.

500 psec input slope

P_{sc} as a Function of Rise/Fall Times

 

When load capacitance is small ($t_{sin}/t_{sout} > 2$ for $V_{DD} > 2\text{ V}$) the power is dominated by P_{sc}


If $V_{DD} < V_{Tn} + |V_{Tp}|$ then P_{sc} is eliminated since both devices are never on at the same time.

$W/L_p = 1.125\text{ }\mu\text{m}/0.25\text{ }\mu\text{m}$
 $W/L_n = 0.375\text{ }\mu\text{m}/0.25\text{ }\mu\text{m}$
 $C_L = 30\text{ fF}$

Digital IC

normalized wrt zero input rise-time dissipation

Leakage (Static) Power Consumption

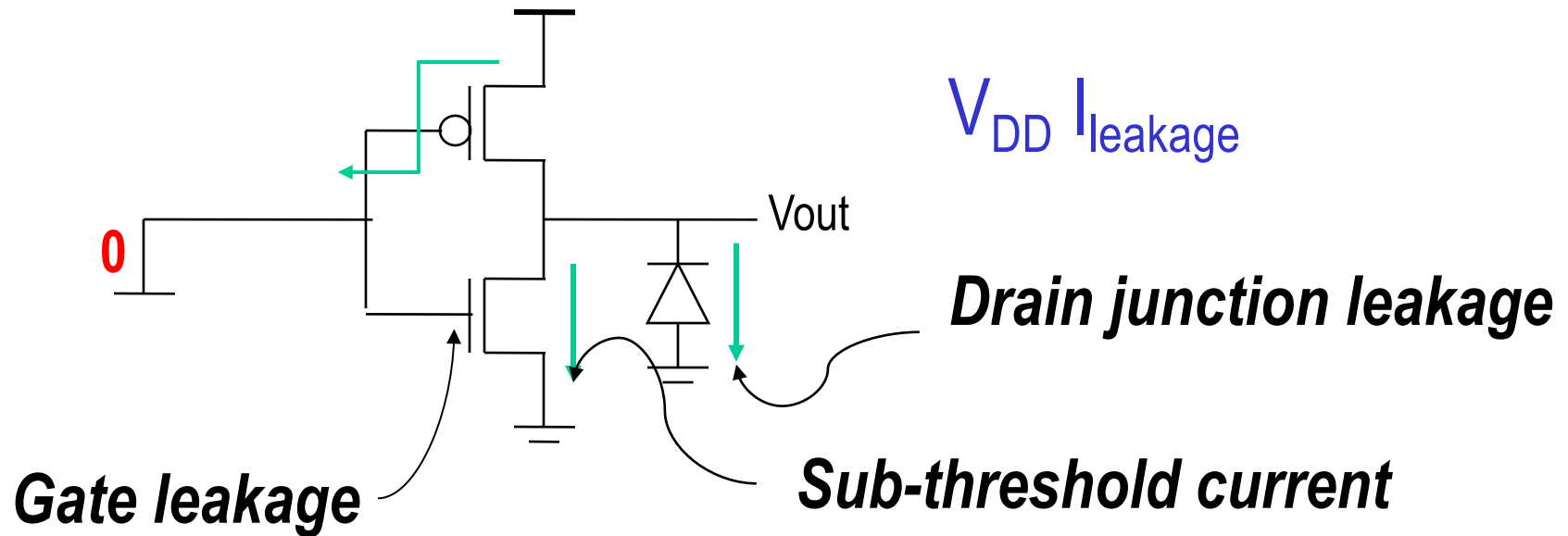

***Sub-threshold current is the dominant factor.
All increase exponentially with temperature!***

Technology Scaling Models

- ***Full scaling(constant electrical)***
 - Ideal model –dimensions and voltage scale together by the same factor S
- ***Fixed voltage scaling***
 - Most common model until recently- only dimensions scale, voltages remain constant
- ***General scaling***
 - Most realistic for today's situation-voltages and dimensions scale with different factors

Scaling Relationships for Long Channel Devices

Parameter	Relation	Full Scaling	General Scaling	Fixed Voltage Scaling
W, L, t_{ox}		$1/S$	$1/S$	$1/S$
V_{DD}, V_T		$1/S$	$1/U$	1
N_{SUB}	V/W_{depl}^2	S	S^2/U	S^2
Area/Device	WL	$1/S^2$	$1/S^2$	$1/S^2$
C_{ox}	$1/t_{ox}$	S	S	S
C_L	$C_{ox}WL$	$1/S$	$1/S$	$1/S$
k_n, k_p	$C_{ox}W/L$	S	S	S
I_{av}	$k_{n,p} V^2$	$1/S$	S/U^2	S
t_p (intrinsic)	$C_L V / I_{av}$	$1/S$	U/S^2	$1/S^2$
P_{av}	$C_L V^2 / t_p$	$1/S^2$	S/U^3	S
PDP	$C_L V^2$	$1/S^3$	$1/SU^2$	$1/S$

Difference between long and short channels

$$I_{Dsat} = \frac{k'_n}{2} \frac{W}{L} (V_{GS} - V_T)^2$$

$$I_D \Big|_{V_{DS}=V_{DSAT}} = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_T) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right]$$
$$= v_{sat} C_{ox} W (V_{GT} - \frac{V_{DSAT}}{2})$$

Transistor Scaling (velocity-saturated devices)

Parameter	Relation	Full Scaling	General Scaling	Fixed-Voltage Scaling
W, L, t_{ox}		$1/S$	$1/S$	$1/S$
V_{DD}, V_T		$1/S$	$1/U$	1
N_{SUB}	V/W_{depl}^2	S	S^2/U	S^2
Area/Device	WL	$1/S^2$	$1/S^2$	$1/S^2$
C_{ox}	$1/t_{ox}$	S	S	S
C_{gate}	$C_{ox}WL$	$1/S$	$1/S$	$1/S$
k_n, k_p	$C_{ox}W/L$	S	S	S
I_{sat}	$C_{ox}WV$	$1/S$	$1/U$	1
Current Density	$I_{sat}/Area$	S	S^2/U	S^2
R_{on}	V/I_{sat}	1	1	1
Intrinsic Delay	$R_{on}C_{gate}$	$1/S$	$1/S$	$1/S$
P	$I_{sat}V$	$1/S^2$	$1/U^2$	1
Power Density	$P/Area$	1	S^2/U^2	S^2